

---

# VCO Fundamentals

**John McNeill**

**Worcester Polytechnic Institute**

`mcneill@ece.wpi.edu`

# Overview

---

- **Functional Block Concept**
- **Oscillator Review**
- **Basic Performance Metrics**
- **Methods of Tuning**
- **Advanced Performance Metrics**
- **Conclusion**


# Overview

---


- **Functional Block Concept**
  - **Applications**
  - **Specifications**
- **Oscillator Review**
- **Basic Performance Metrics**
- **Methods of Tuning**
- **Advanced Performance Metrics**
- **Conclusion**
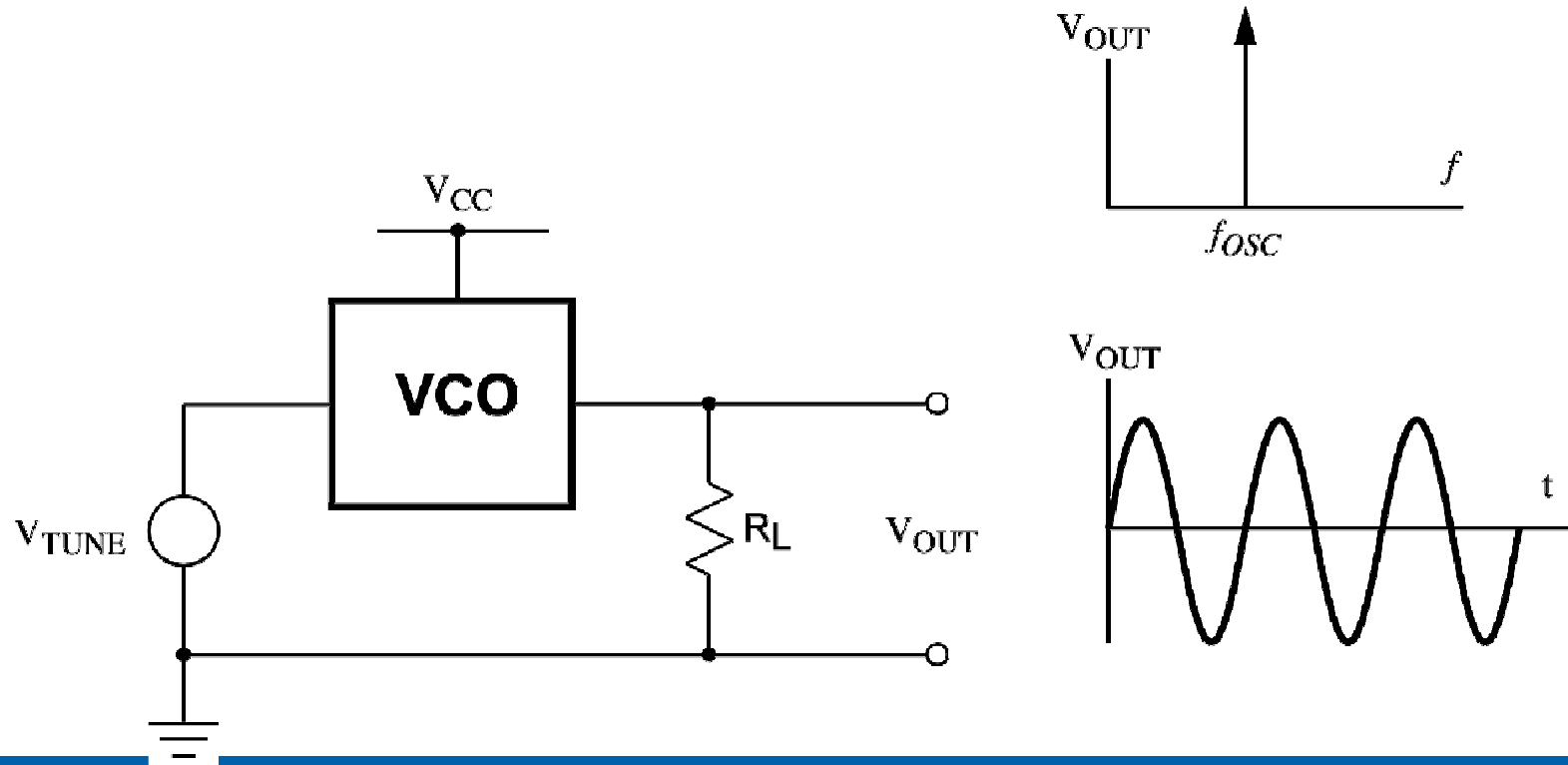
# Functional Block Concept

- Input control voltage  $V_{TUNE}$  determines frequency of output waveform




# Applications: RF System

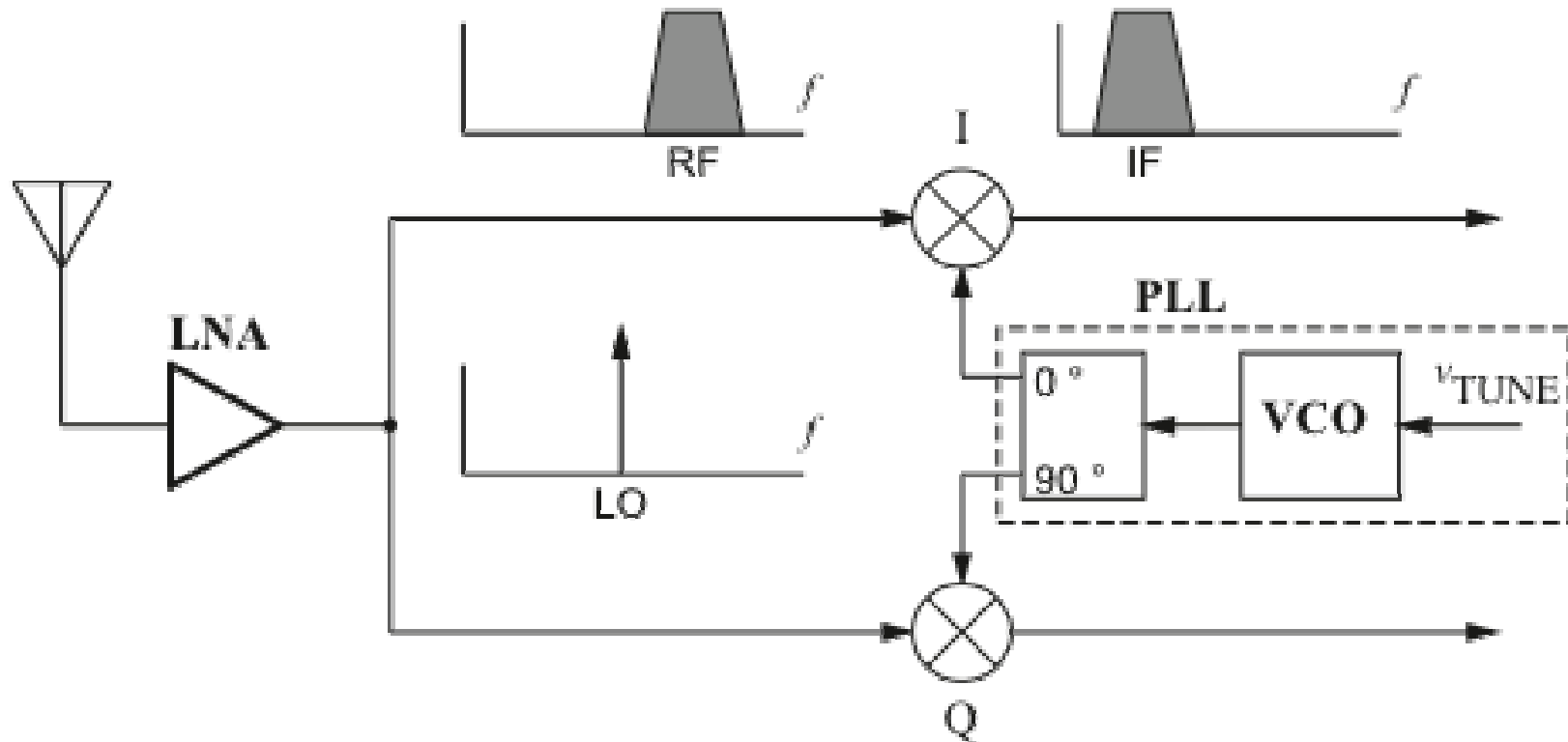

- Downconvert band of interest to IF
- VCO: Electrically tunable selection

# Applications: Digital System

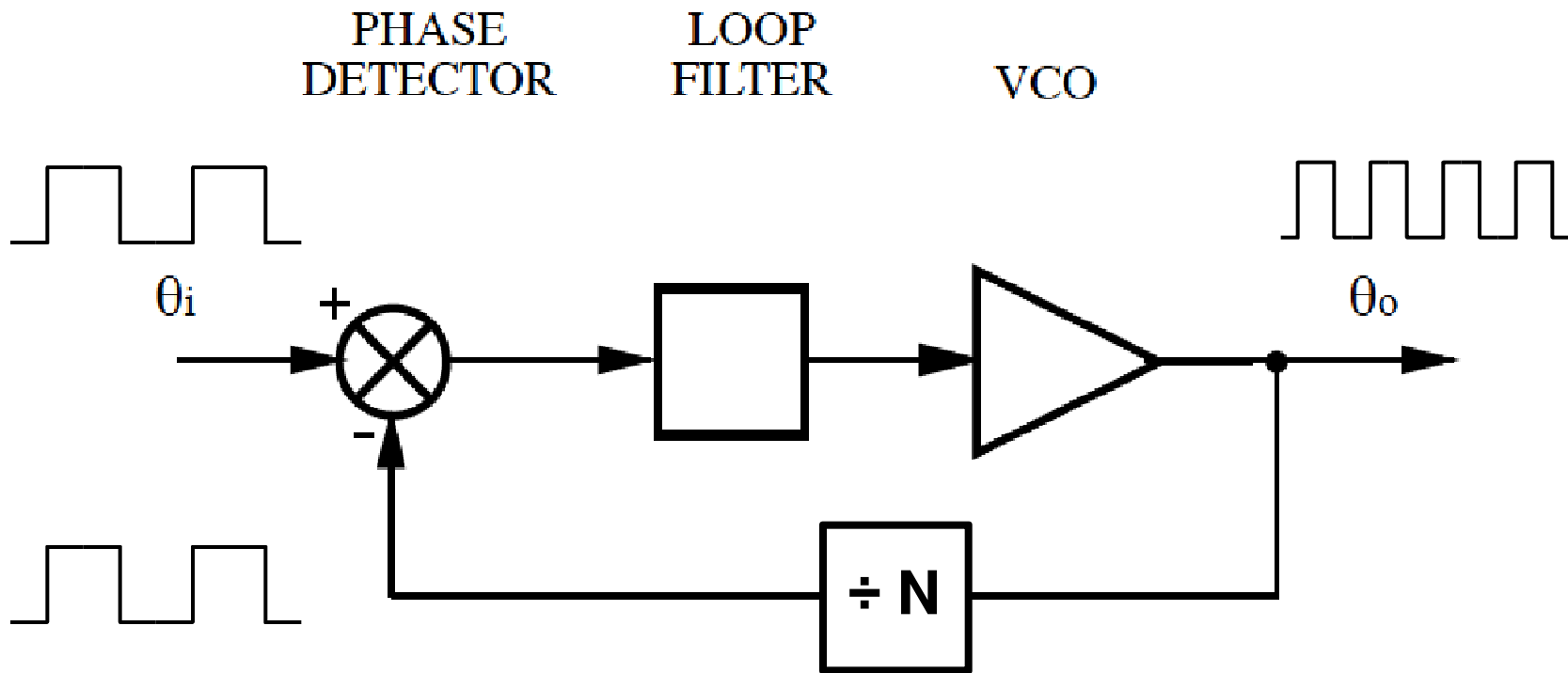

- **Clock synthesis (frequency multiplication)**

J. A. McNeill and D. R. Ricketts, "The Designer's Guide to Jitter in Ring Oscillators." Springer, 2009

# Specifications

## VOLTAGE CONTROLLED OSCILLATORS 50 Ω

12.5 MHz to 3 GHz



MODEL PREFIX	FREQUENCY (MHz)		POWER OUTPUT (dBm)	TUNE VOLTAGE (V)		PHASE NOISE (dBc/Hz) SSB@ offset frequencies: Typ.				PULLING (MHz) pk-pk @12 dB	PUSHING (MHz/V)	TUNING SENSITIVITY (MHz/V)	HARMONICS (dBc)		3dB MOD. BANDWIDTH (kHz)	POWER SUPPLY	
	Min.	Max.		Typ.	Min.	Max.	1 kHz	10 kHz	100 kHz				1 MHz	Typ.		Max.	Typ.

### LINEAR TUNING Wideband

JCOS-175LN	125	175	+3.7	1.0	17.0	-95	-118	-138	-158	0.08	0.05	3-5	-25	-20	2900	12.0	20
JCOS-820BLN	807	832	+3.0	1.0	14.0	-88	-112	-132	-151	0.4	0.4	6.0	-24	-20	2000	10.0	25
JCOS-820WLN	780	860	+9.0	0.0	20.0	-90	-112	-132	-150	4.5	0.3	8.0	-13	-8	2000	9.0	25
JCOS-1110LN	1079	1114	+8.5	0.0	20.0	-88	-110	-130	-150	7.5	0.5	4.5	-15	-10	2000	8.0	25
JTOS-25	12.5	25	+8.0	1.0	11.0	-95	-115	-135	-155	0.03	0.02	1.0-4.0	-26	-13	130	12.0	20
JTOS-50	25	47	+8.5	1.0	15.0	-88	-108	-127	-147	0.06	0.04	2.0-2.6	-19	-12	50	12.0	20
JTOS-75	37.5	75	+8.0	1.0	16.0	-89	-110	-130	-140	0.15	0.11	2.8-4.0	-27	-20	125	12.0	20
JTOS-100	50	100	+8.3	1.0	16.0	-83	-108	-128	-140	0.6	0.2	3.7-4.8	-35	-20	100	12.0	18
JTOS-150	75	150	+9.5	1.0	16.0	-82	-106	-127	-147	0.8	0.3	5.8-6.7	-23	-17	112	12.0	20
JTOS-200	100	200	+10.0	1.0	16.0	-84	-105	-124	-145	1.0	0.2	6-10	-25	-20	110	12.0	20
JTOS-300	150	280	+9.0	1.0	16.0	-82	-102	-122	-142	1.0	0.2	9-14	-28	-20	120	12.0	20
JTOS-400	200	380	+9.0	1.0	16.0	-82	-102	-122	-142	1.4	0.4	10.5-17.1	-25	-20	130	12.0	20
JTOS-535	300	525	+9.5	1.0	16.0	-75	-97	-117	-137	2.0	0.5	10-24	-28	-20	115	12.0	20
JTOS-765	485	765	+8.0	1.0	16.0	-75	-98	-118	-138	2.0	0.5	20-30	-30	-20	100	12.0	20
JTOS-850VW	400	850	+6.0	0.5	18.0	-74	-96	-116	-136	6.0	1.5	15-80	-20	—	185	5.0	20
JTOS-1000W	500	1000	+7.0	1.0	18.0	-73	-94	-114	-134	5.0	1.0	30-40	-26	-20	100	12.0	25

# Overview

---

- **Functional Block Concept**
- **Oscillator Review**
  - **Frequency Control**
  - **Amplitude Control**
  - **Types of Oscillators**
- **Basic Performance Metrics**
- **Methods of Tuning**
- **Advanced Performance Metrics**
- **Conclusion**




# Oscillator Review

---



- **Types of Oscillators**
  - Multivibrator
  - Ring
  - Resonant
  - Feedback
- **Basic Factors in Oscillator Design**
  - Frequency
  - Amplitude / Output Power
  - Startup

# Multivibrator

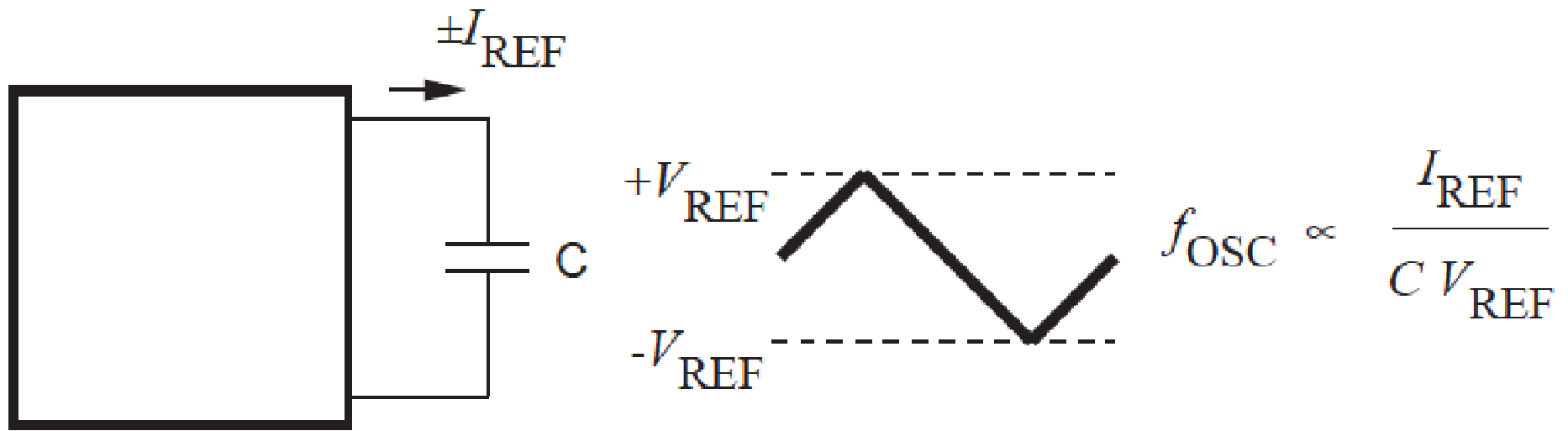



- **Conceptual multivibrator oscillator**
  - Also called astable or relaxation oscillator
- **One energy storage element**

# Example: Multivibrator

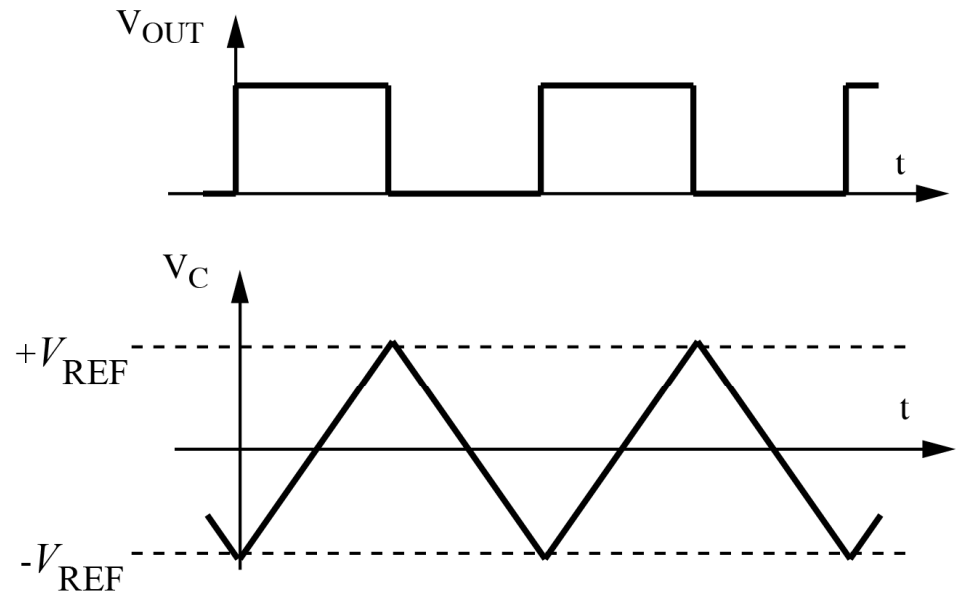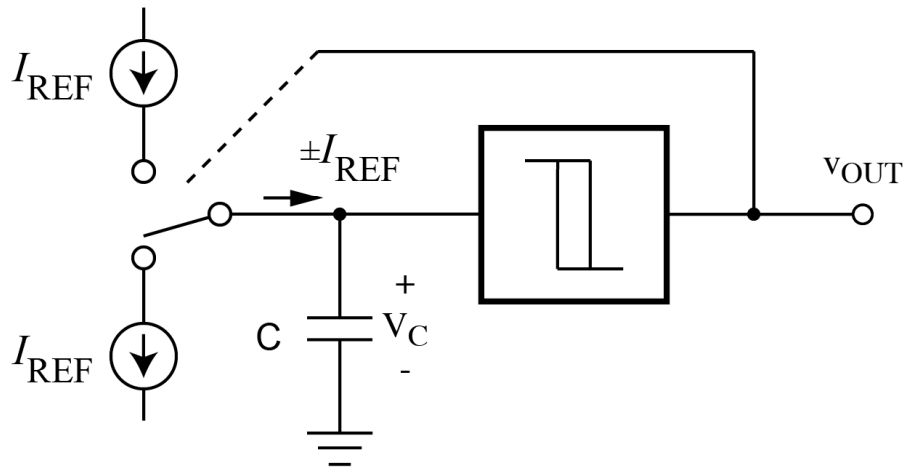

- **Frequency:** Controlled by charging current  $I_{REF}$ ,  $C$ ,  $V_{REF}$  thresholds
- **Amplitude:** Controlled by thresholds, logic swing
- **Startup:** Guaranteed; no stable state

# Ring Oscillator

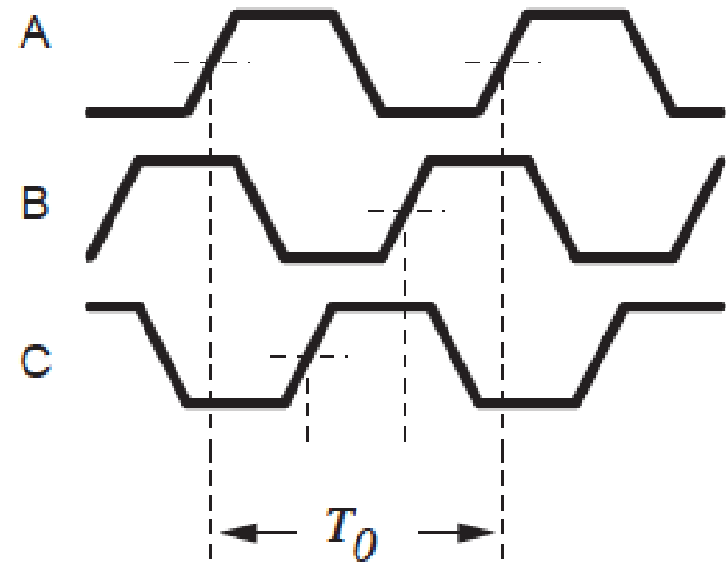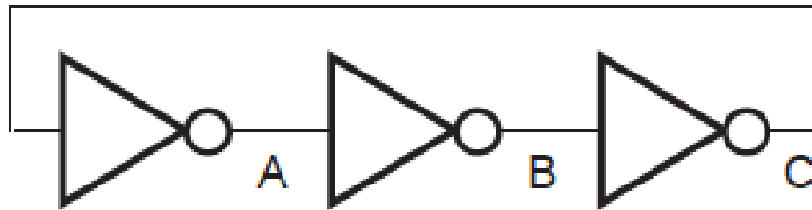


- **Frequency: Controlled by gate delay**
- **Amplitude: Controlled by logic swing**
- **Startup: Guaranteed; no stable state**


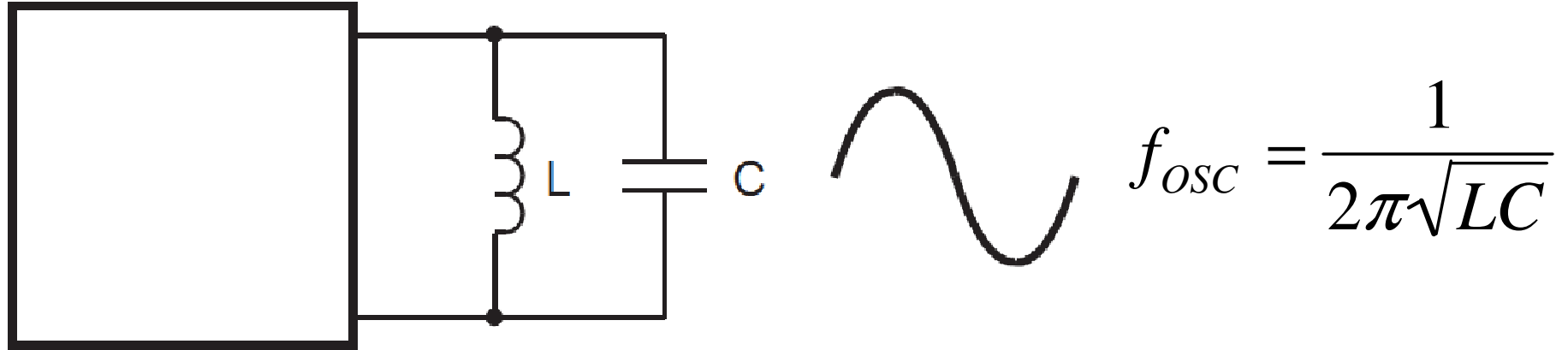
# Resonant Oscillator

---

- **Concept: Natural oscillation frequency of resonance**
- **Energy flows back and forth between two storage modes**




# Resonant Oscillator (Ideal)

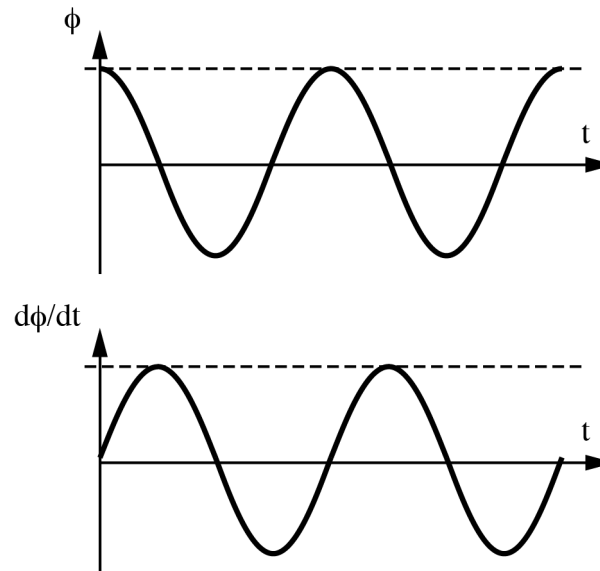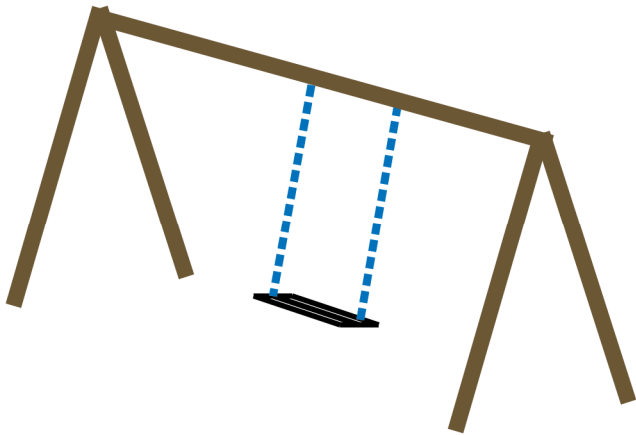


- **Example: swing (ideal)**
- **Energy storage modes: potential, kinetic**
- **Frequency: Controlled by length of pendulum**
- **Amplitude: Controlled by initial position**
- **Startup: Needs initial condition energy input**

# Resonant Oscillator (Real)

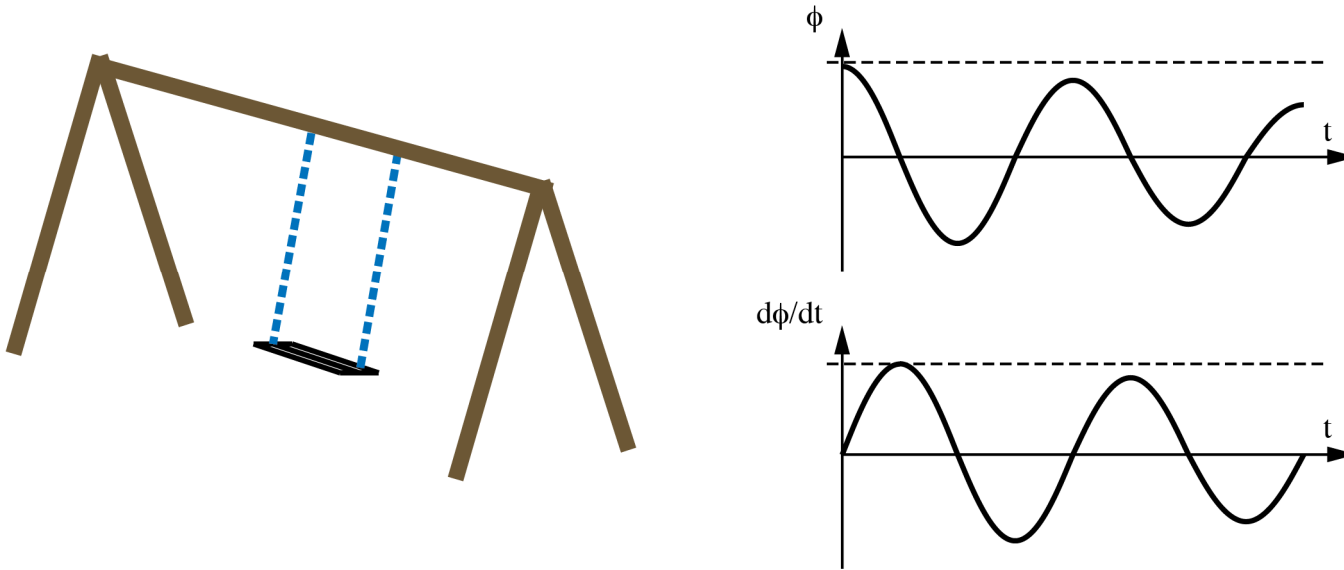

- **Problem: Loss of energy due to friction**
- **Turns “organized” energy (potential, kinetic) into “disorganized” thermal energy (frictional heating)**
- **Amplitude decays toward zero**
- **Requires energy input to maintain amplitude**
- **Amplitude controlled by “supervision”**


# LC Resonant Oscillator (Ideal)

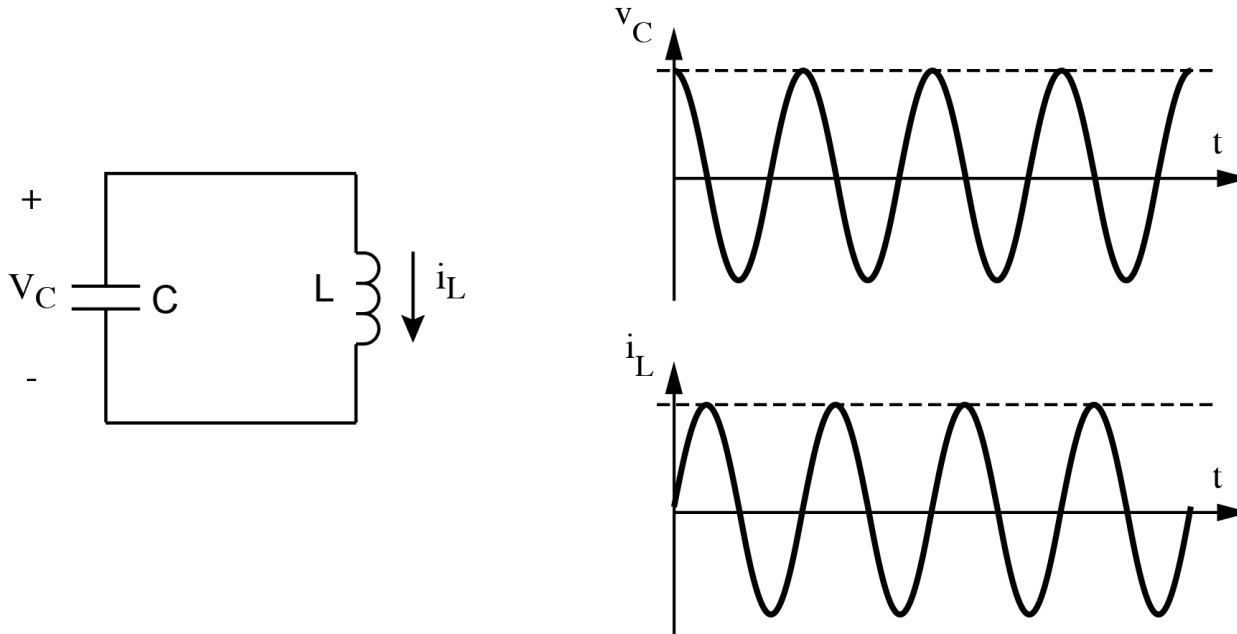

- **Energy storage modes:**  
Magnetic field (L current), Electric field (C voltage)
- **Frequency: Controlled by LC**
- **Amplitude: Controlled by initial condition**
- **Startup: Needs initial energy input (initial condition)**




# LC Resonant Oscillator (Real)

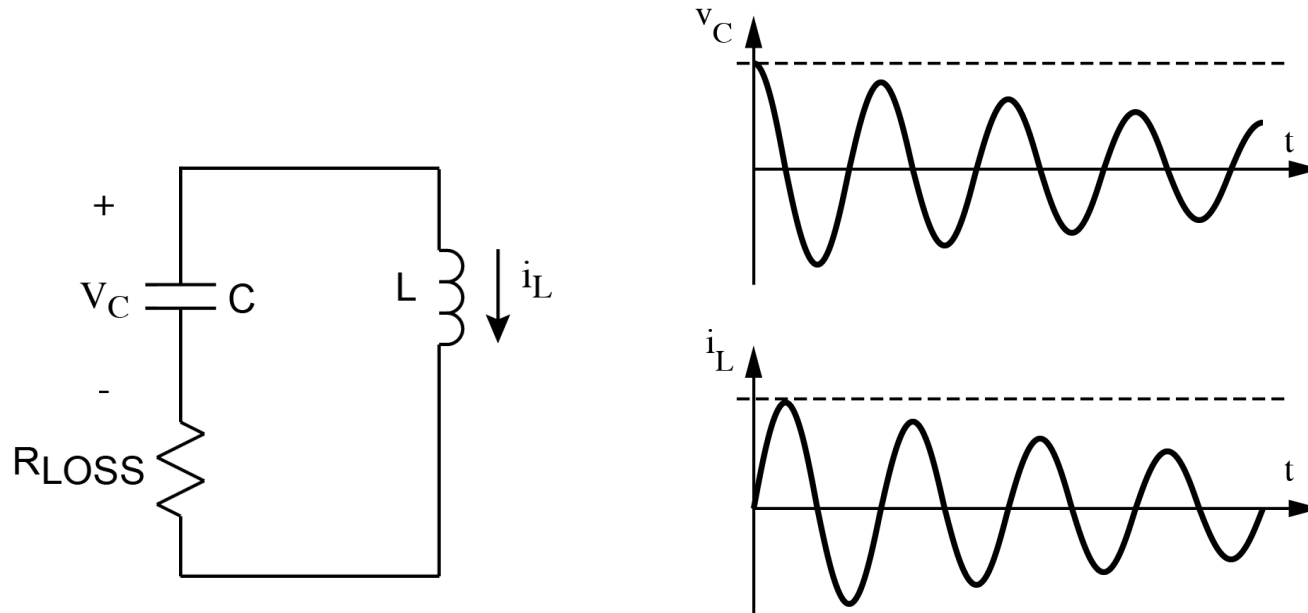

- **Problem: Loss of energy due to nonideal L, C**
  - Model as resistor  $R_{LOSS}$ ; Q of resonator
- **E, M field energy lost to resistor heating**
- **Amplitude decays toward zero**


# LC Resonant Oscillator (Real)

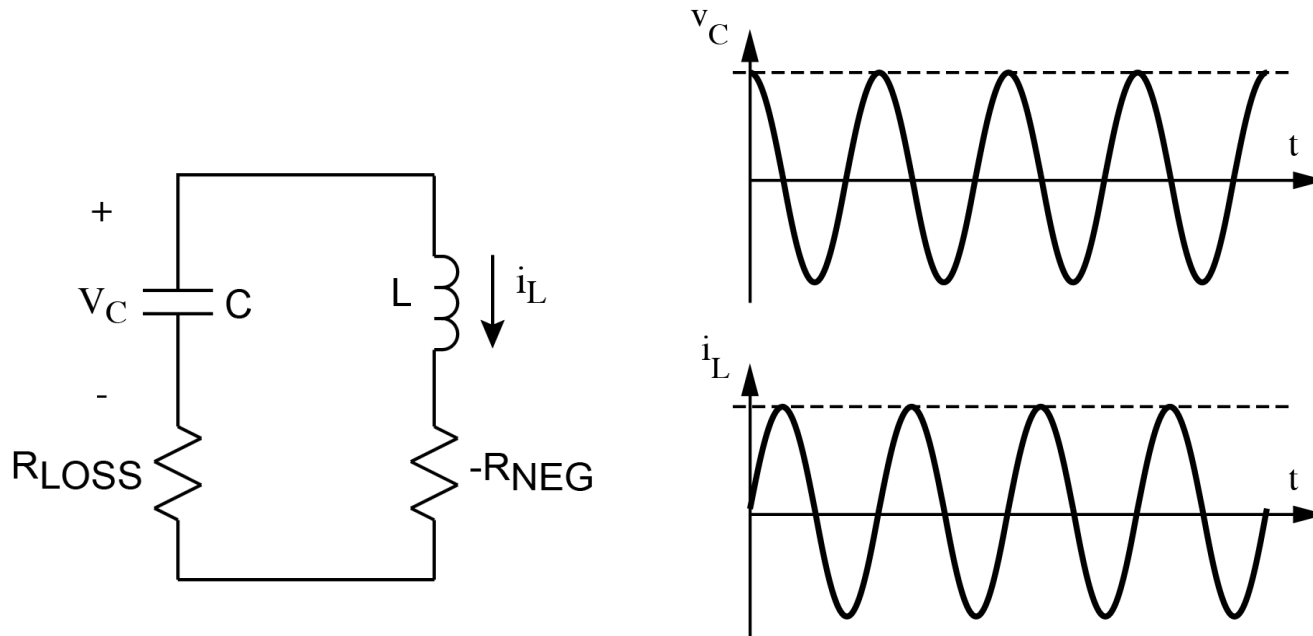

- **Problem: Loss of energy due to nonideal L, C**
- **Requires energy input to maintain amplitude**
- **Synthesize “negative resistance”**
- **Cancel  $R_{LOSS}$  with  $-R_{NEG}$**



# Negative Resistance

---

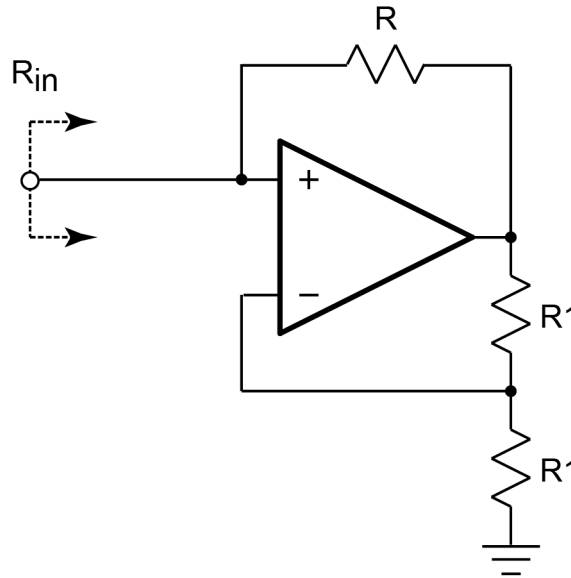


- Use active device to synthesize V-I characteristic that “looks like”  $-R_{NEG}$
- Example: amplifier with positive feedback
- Feeds energy into resonator to counteract losses in  $R_{LOSS}$


# Feedback Oscillator: Wien Bridge

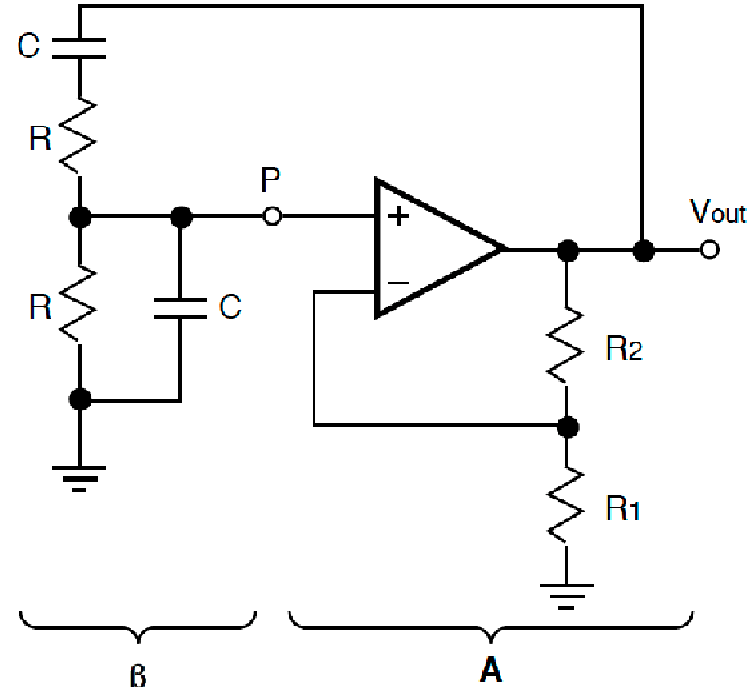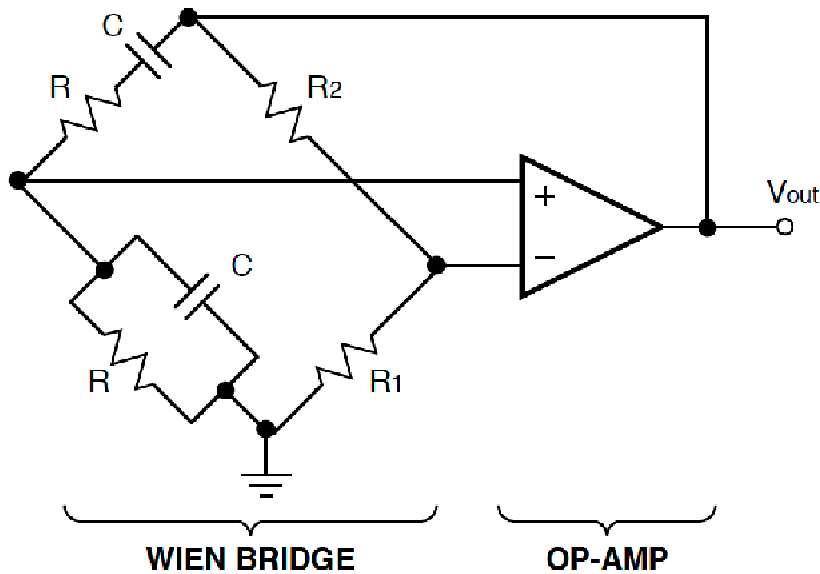


- **Forward gain  $A=3$**
- **Feedback network with transfer function  $\beta(f)$**
- **At  $f_{osc}$ ,  $|\beta|=1/3$  and  $\angle \beta = 0$**
- **Thought experiment: break loop, inject sine wave, look at signal returned around feedback loop**

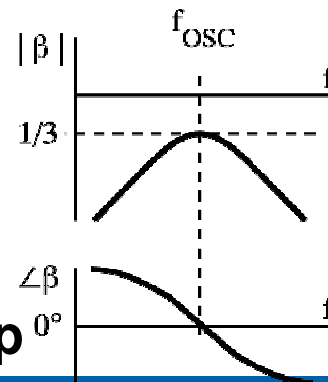


# $A\beta=1$

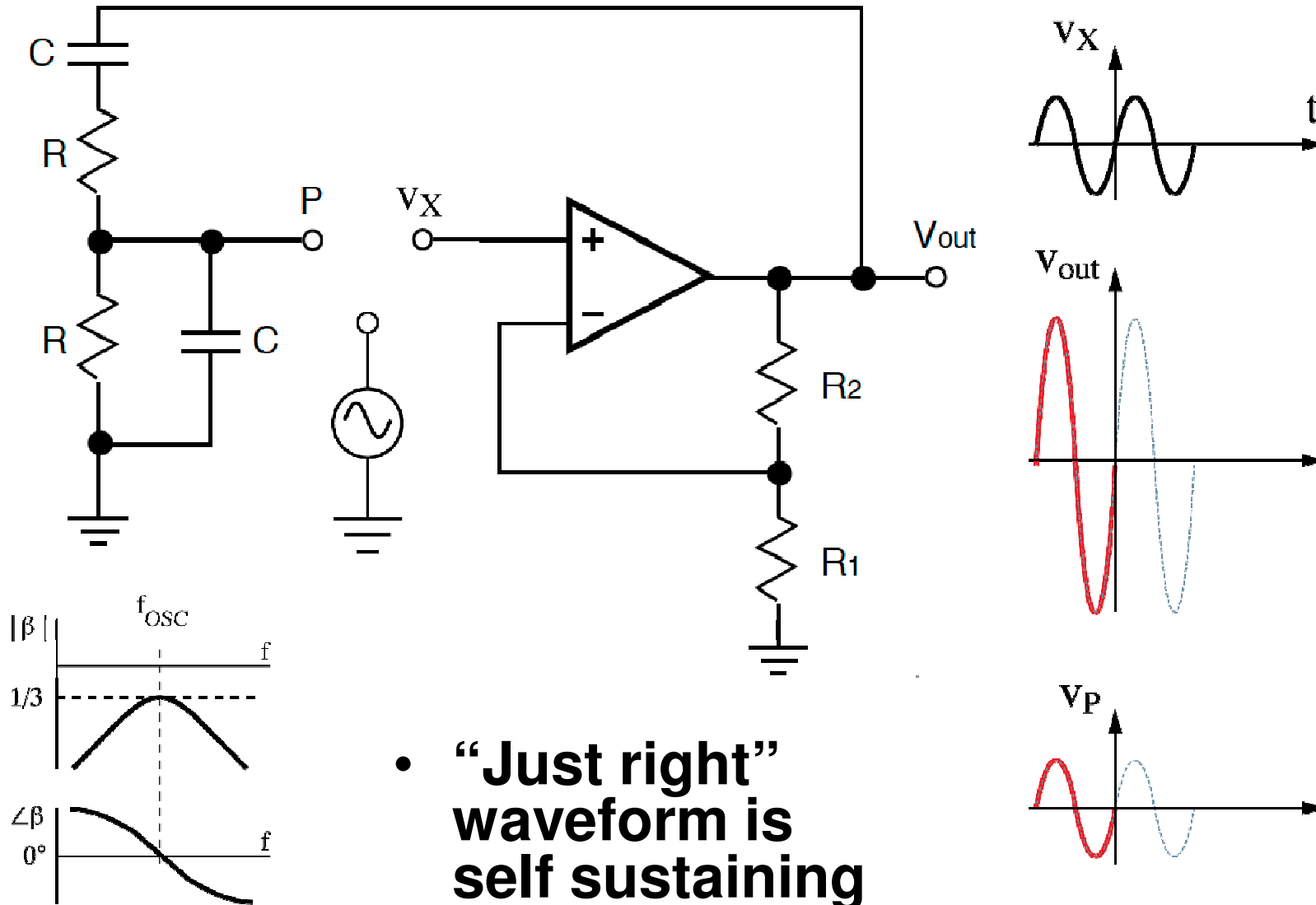


# $A\beta = 0.99$

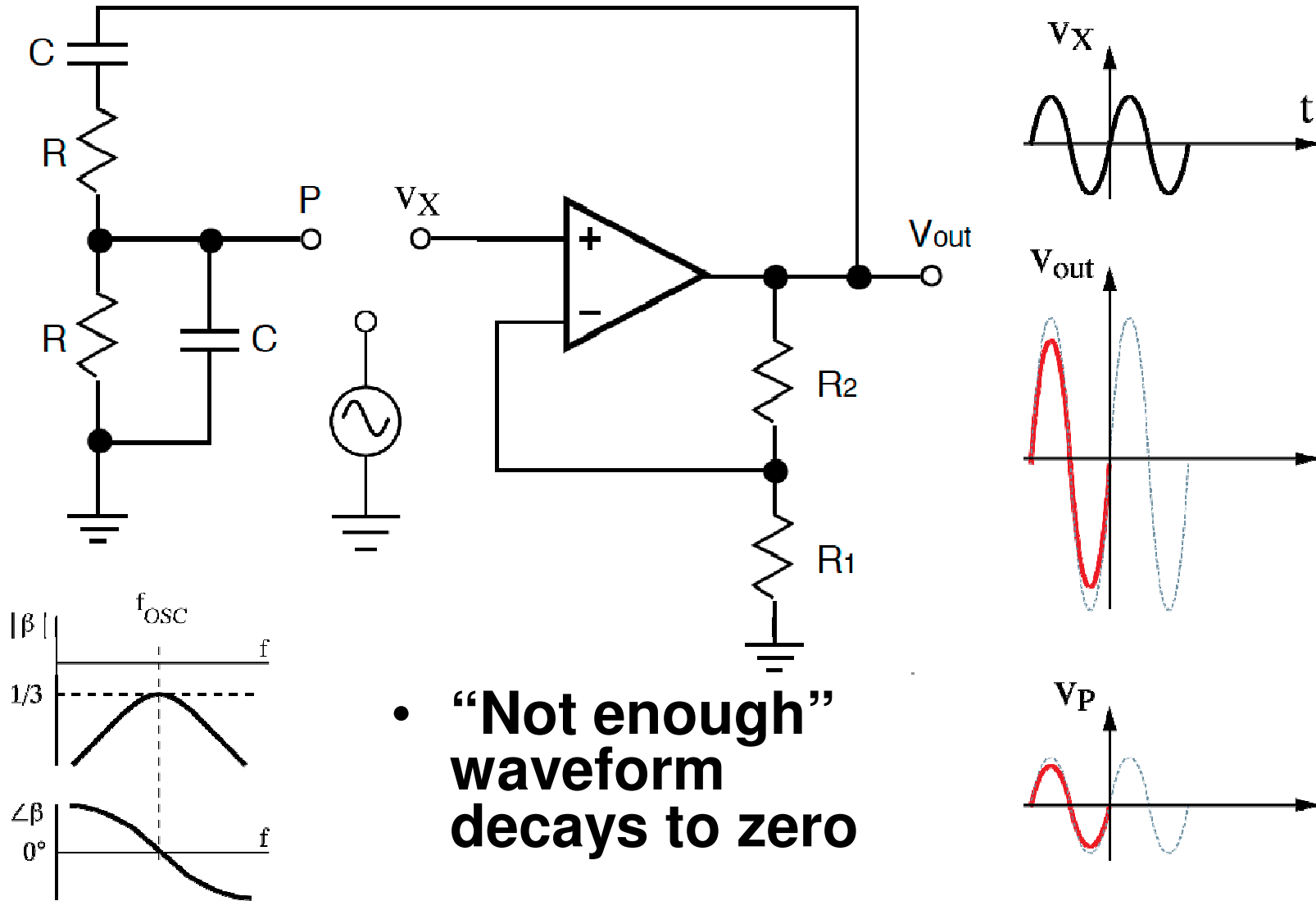

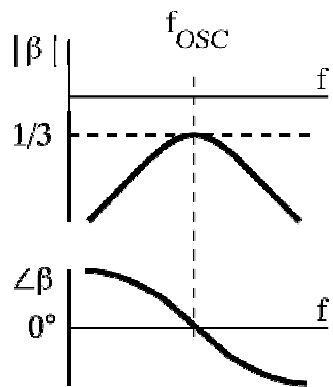
- **“Not enough” waveform decays to zero**



# $A\beta = 1.01$

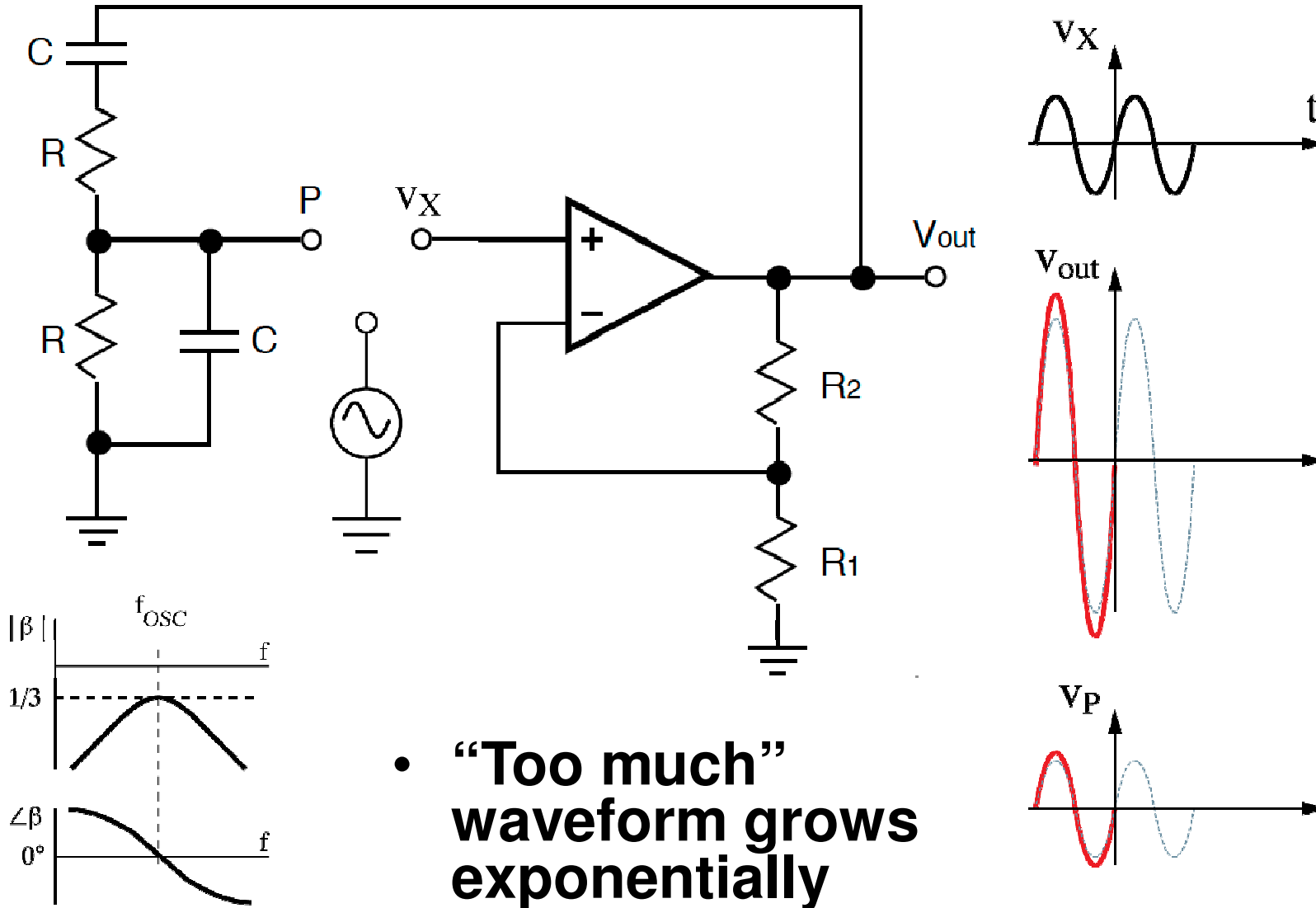



# Feedback oscillator

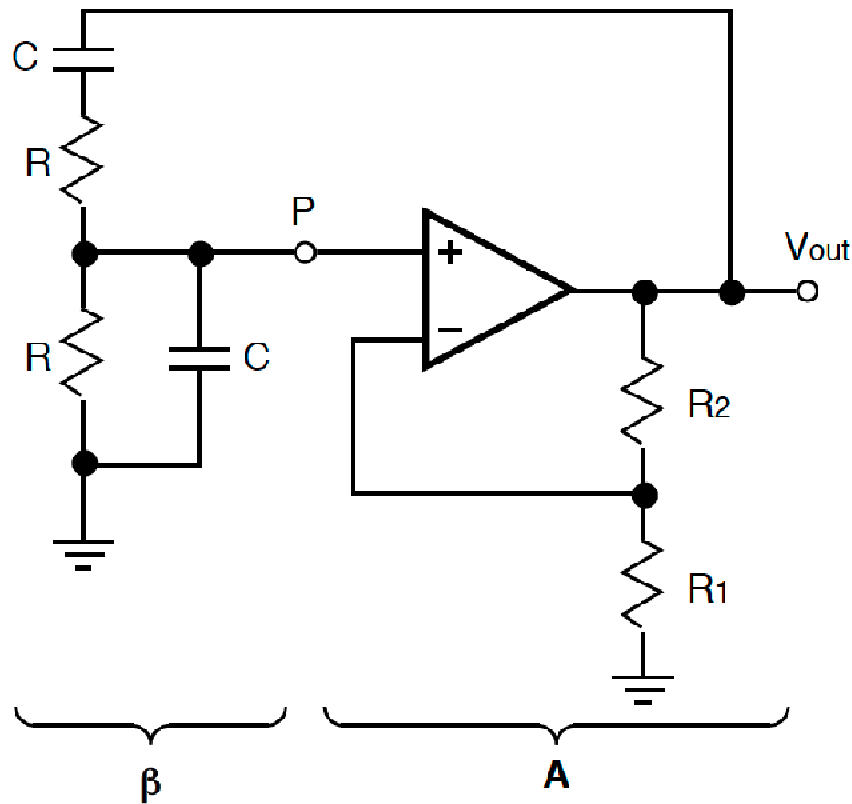


- **Stable amplitude condition:  $A\beta=1$  EXACTLY**
- **Frequency determined by feedback network  $A\beta=1$  condition**
- **Need supervisory circuit to monitor amplitude**
- **Startup: random noise; supervisory circuit begins with  $A\beta>1$**




# Resonant Oscillator (Real)

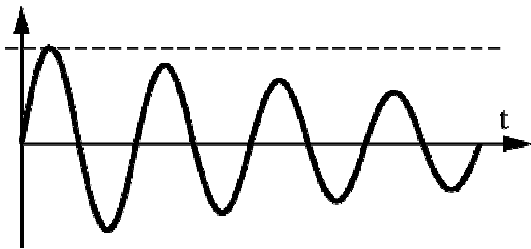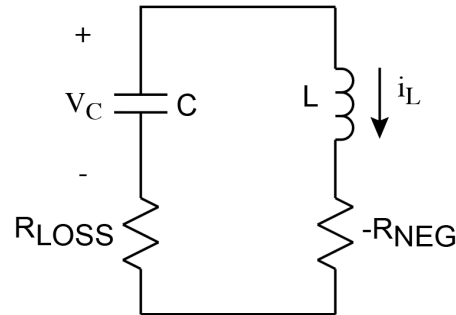

$$|R_{\text{NEG}}| < R_{\text{LOSS}}$$

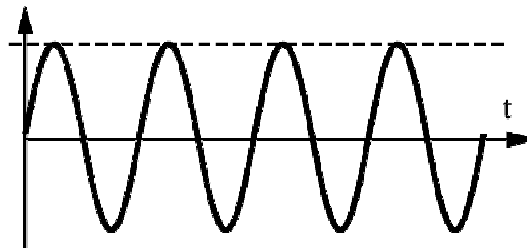

$$|R_{\text{NEG}}| = R_{\text{LOSS}}$$

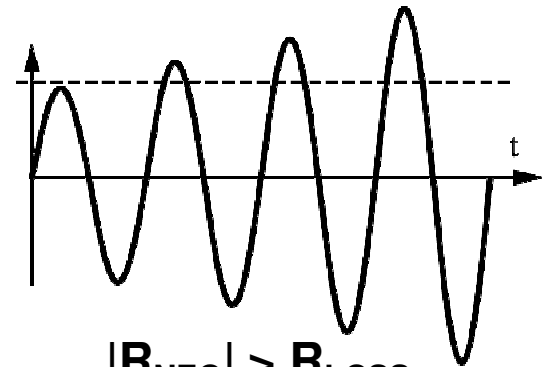


$$|R_{\text{NEG}}| > R_{\text{LOSS}}$$

- **Stable amplitude condition:  $|R_{\text{NEG}}| = R_{\text{LOSS}}$  EXACTLY**
- **Frequency determined by LC network**
- **Startup: random noise; begin with  $|R_{\text{NEG}}| > R_{\text{LOSS}}$**
- **Amplitude grows; soft clip gives average  $|R_{\text{NEG}}| = R_{\text{LOSS}}$**
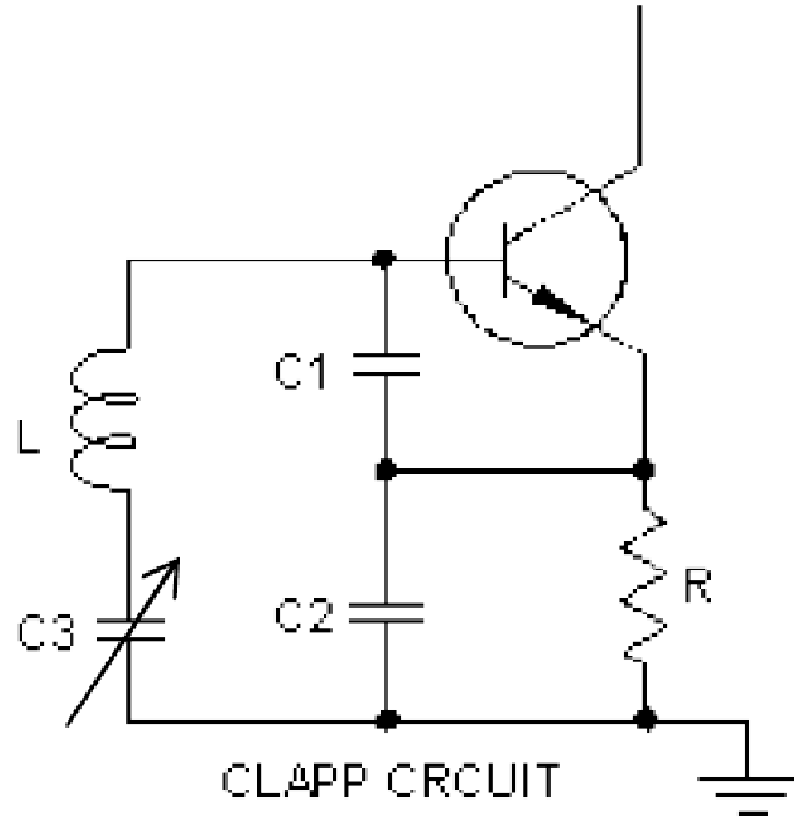
# Clapp oscillator


$$f_{osc} = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$C_{eq} = \frac{1}{\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}\right)}$$



- **L, C1-C2-C3 set oscillation frequency  $f_{osc}$**

# Clapp oscillator

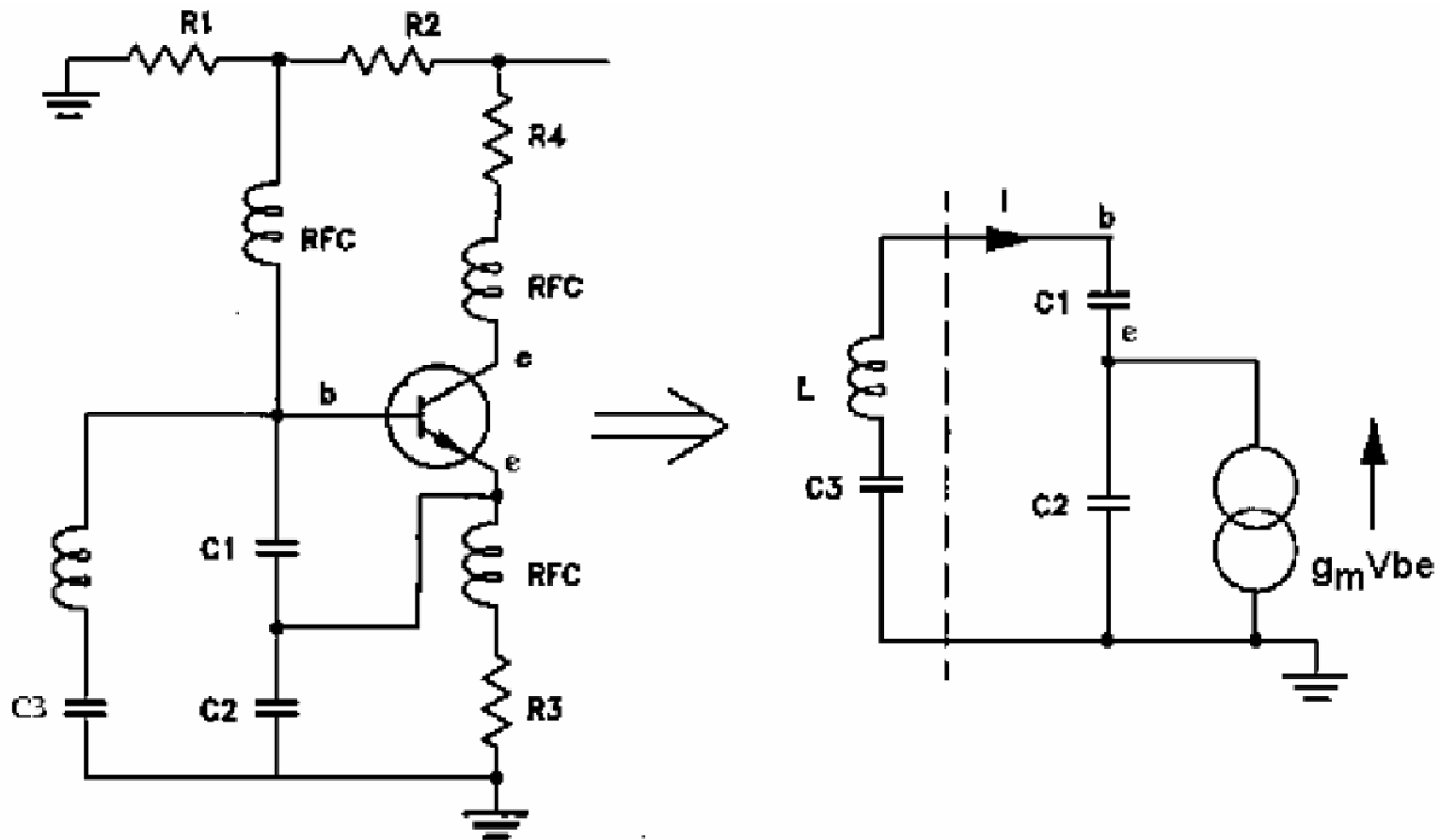


- **Circuit configuration**


- **Equivalent circuit**

MiniCircuits AN95-007, "Understanding Oscillator Concepts"

# Clapp oscillator

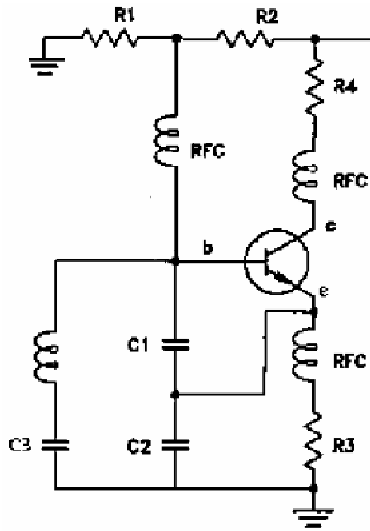

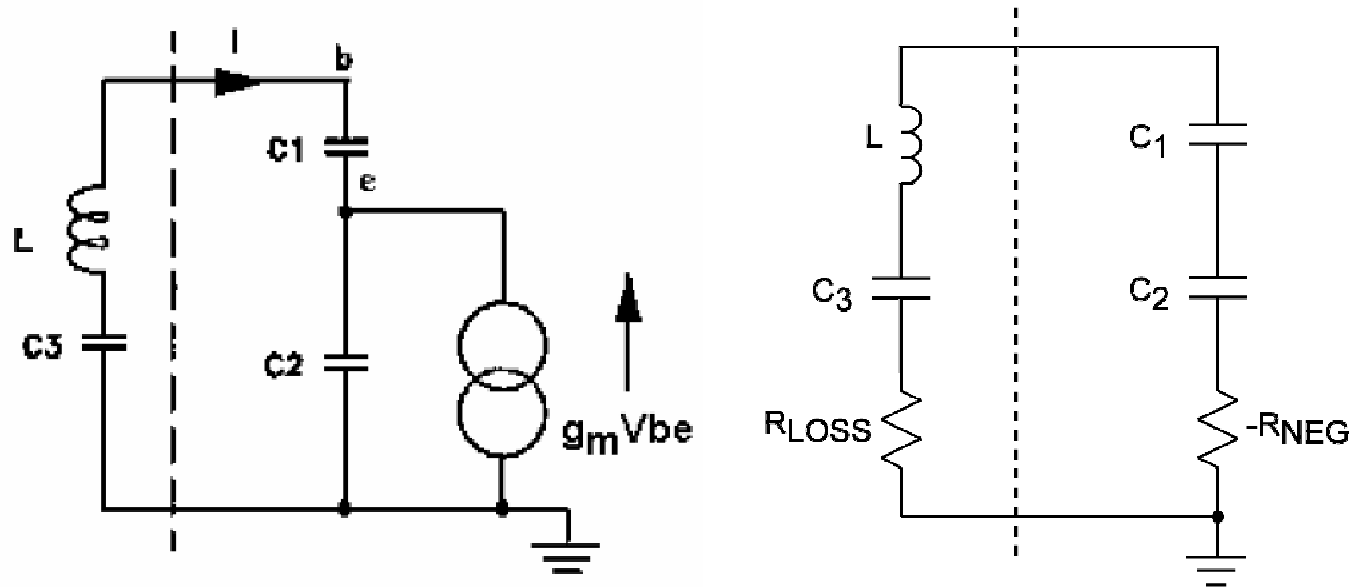
$$Z_{eq} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} - \frac{g_m}{\omega^2 C_1 C_2}$$



- **Frequency:** Determined by L, C1, C2, C3
- **Amplitude:** Grows until limited by  $g_m$  soft clipping
- **Startup:** Choose C1, C2 feedback for  $|R_{NEG}| > R_{LOSS}$
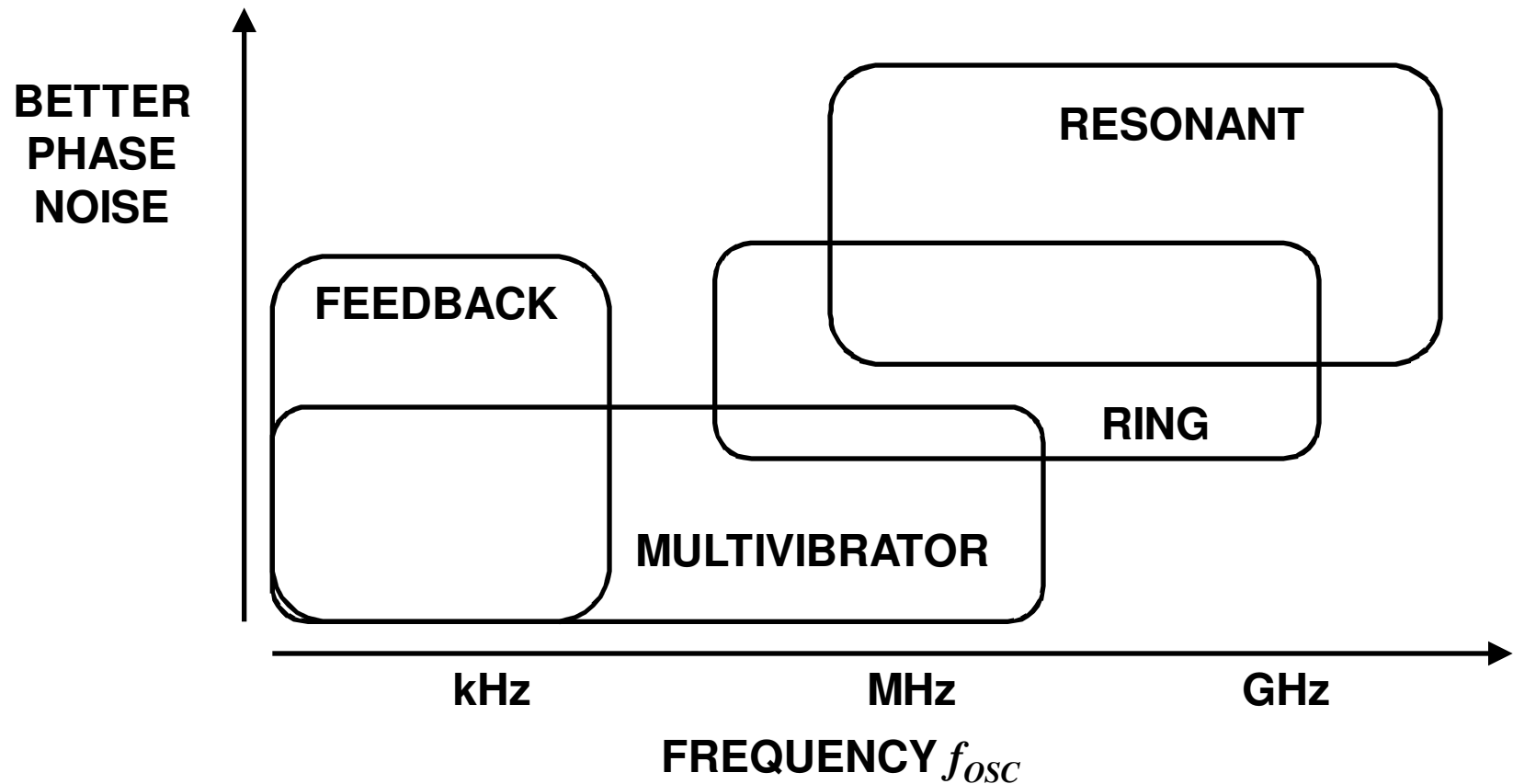
# Oscillator Summary

- Typical performance of oscillator architectures:



# Overview

---

- Functional Block Concept
- Oscillator Review
- **Basic Performance Metrics**
  - Frequency Range
  - Tuning Range
- Methods of Tuning
- Advanced Performance Metrics
- Conclusion

# Basic Performance Metrics

## VOLTAGE CONTROLLED OSCILLATORS 50 Ω

12.5 MHz to 3 GHz



MODEL PREFIX	FREQUENCY (MHz)		POWER OUTPUT (dBm)	TUNE VOLTAGE (V)		PHASE NOISE (dBc/Hz) SSB@ offset frequencies: Typ.				PULLING (MHz) pk-pk @12 dB	PUSHING (MHz/V)	TUNING SENSITIVITY (MHz/V)	HARMONICS (dBc)		3dB MOD. BANDWIDTH (kHz)	POWER SUPPLY	
	Min.	Max.		Min.	Max.	1 kHz	10 kHz	100 kHz	1 MHz				Typ.	Max.		Typ.	Max.

### LINEAR TUNING Wideband

JCOS-175LN	125	175	+3.7	1.0	17.0	-95	-118	-138	-158	0.08	0.05	3-5	-25	-20	2900	12.0	20
JCOS-820BLN	807	832	+3.0	1.0	14.0	-88	-112	-132	-151	0.4	0.4	6.0	-24	-20	2000	10.0	25
JCOS-820WLN	780	860	+9.0	0.0	20.0	-90	-112	-132	-150	4.5	0.3	8.0	-13	-8	2000	9.0	25
JCOS-11100LN	1079	1114	+8.5	0.0	20.0	-88	-110	-130	-150	7.5	0.5	4.5	-15	-10	2000	8.0	25
JTOS-25	12.5	25	+8.0	1.0	11.0	-95	-115	-135	-155	0.03	0.02	1.0-4.0	-26	-13	130	12.0	20
JTOS-50	25	47	+8.5	1.0	15.0	-88	-108	-127	-147	0.06	0.04	2.0-2.6	-19	-12	50	12.0	20
JTOS-75	37.5	75	+8.0	1.0	16.0	-89	-110	-130	-140	0.15	0.11	2.8-4.0	-27	-20	125	12.0	20
JTOS-100	50	100	+8.3	1.0	16.0	-83	-108	-128	-140	0.6	0.2	3.7-4.8	-35	-20	100	12.0	18
JTOS-150	75	150	+9.5	1.0	16.0	-82	-106	-127	-147	0.8	0.3	5.8-6.7	-23	-17	112	12.0	20
JTOS-200	100	200	+10.0	1.0	16.0	-84	-105	-124	-145	1.0	0.2	6-10	-25	-20	110	12.0	20
JTOS-300	150	280	+9.0	1.0	16.0	-82	-102	-122	-142	1.0	0.2	9-14	-28	-20	120	12.0	20
JTOS-400	200	380	+9.0	1.0	16.0	-82	-102	-122	-142	1.4	0.4	10.5-17.1	-25	-20	130	12.0	20
JTOS-535	300	525	+9.5	1.0	16.0	-75	-97	-117	-137	2.0	0.5	10-24	-28	-20	115	12.0	20
JTOS-765	485	765	+8.0	1.0	16.0	-75	-98	-118	-138	2.0	0.5	20-30	-30	-20	100	12.0	20
JTOS-850VW	400	850	+6.0	0.5	18.0	-74	-96	-116	-136	6.0	1.5	15-80	-20	—	185	5.0	20
JTOS-1000W	500	1000	+7.0	1.0	18.0	-73	-94	-114	-134	5.0	1.0	30-40	-26	-20	100	12.0	25

# Basic Performance Metrics

Surface Mount

## Voltage Controlled Oscillator

JTOS-1000W+

Wide Band 500 to 1000 MHz

### Features

- wide frequency range, 500 to 1000 MHz typ.
- 3 dB modulation bandwidth 100 kHz typ.
- octave, linear tuning
- low phase noise, -134 dBc/Hz at 1 MHz offset, typ.
- excellent harmonic suppression, -26 dBc typ.
- aqueous washable

### Applications

- test instruments-signal generators
- wideband frequency synthesizers
- agile communications systems
- catv distribution and set-top convertors
- cellular up and down converters
- digital cordless phones



CASE STYLE: BK377  
PRICE: \$21.95 ea. QTY (5-49)

**+RoHS Compliant**


The +Suffix identifies RoHS Compliance. See our web site for RoHS Compliance methodologies and qualifications

### Electrical Specifications

FREQUENCY (MHz)		POWER OUTPUT (dBm)	TUNING VOLTAGE (V)		PHASE NOISE (dBc/Hz) SSB at offset frequencies: Typ.				PULLING pk-pk @ 12 dB (MHz)	PUSHING (MHz/V)	TUNING SENSITIVITY (MHz/V)	HARMONICS (dBc)		3 dB MODULATION BANDWIDTH (MHz)	DC OPERATING POWER	
Min.	Max.	Typ.	Min.	Max.	1 kHz	10 kHz	100 kHz	1 MHz	Typ.	Typ.	Typ.	Typ.	Max.	Typ.	Vcc (volts)	Current (mA) Max.
500	1000	+7.0	1.0	18	-73	-94	-114	-134	5.0	1.0	30-40	-26	-20	0.1	12	25




# Basic Performance Metrics

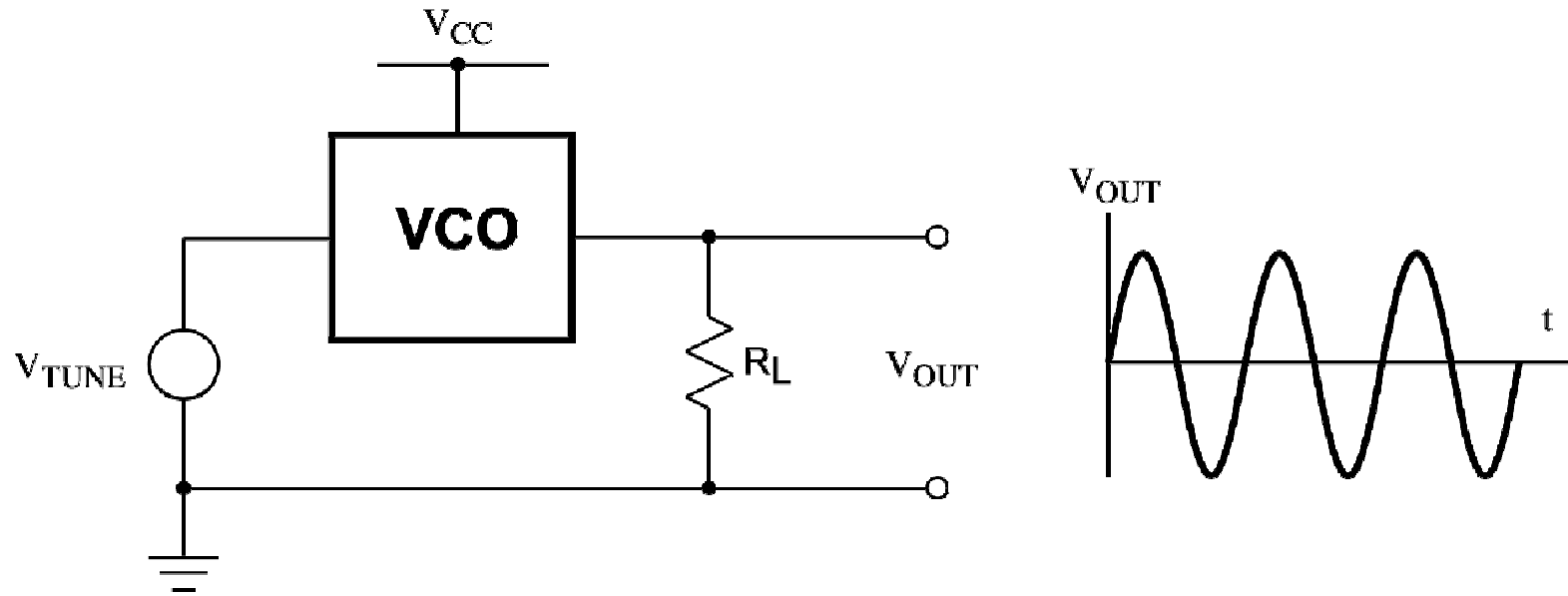

- **Supply:** DC operating power
- **Output**
  - **Sine:** output power dBm into  $50\Omega$
  - **Square:** compatible logic
- **Frequency Range**
- **Tuning Voltage Range**

# Frequency Range

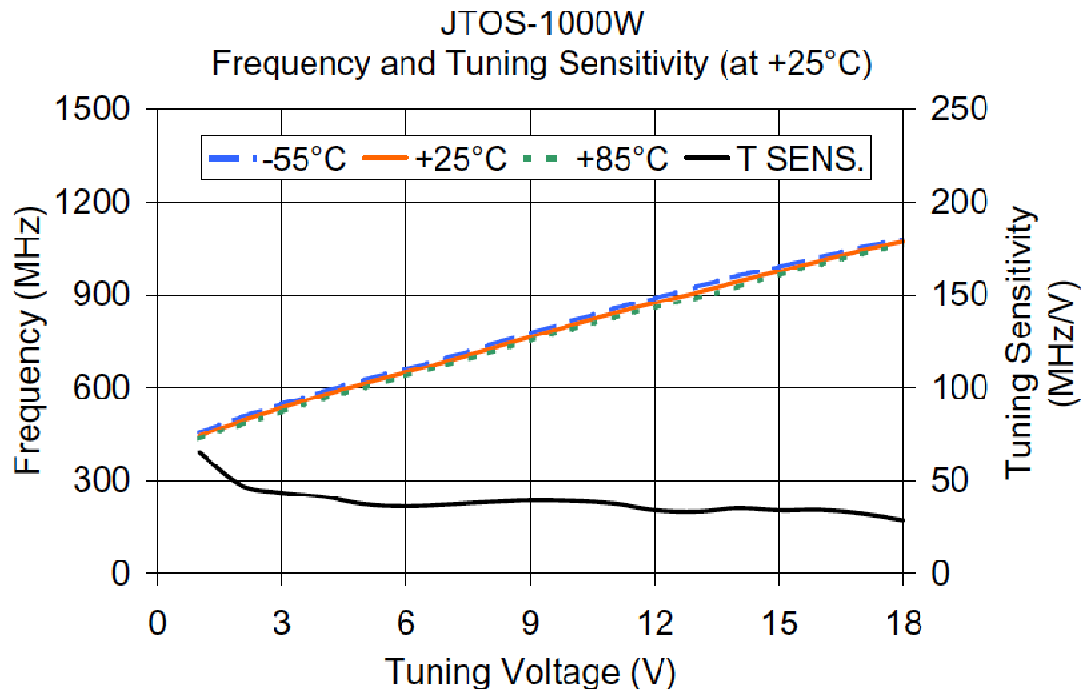

V TUNE	TUNING SENS. (MHz/V)	FREQUENCY (MHz)		
		-55°C	+25°C	+85°C
1.00	65.31	455.40	443.44	433.76
2.00	47.64	503.88	491.08	480.00
3.00	43.38	546.43	534.46	521.76
4.00	41.23	587.53	575.68	562.24
5.00	37.18	624.47	612.87	600.23
6.00	36.00	660.47	648.87	636.80
7.00	36.98	697.54	685.84	673.93
8.00	38.32	736.41	724.17	711.94
9.00	39.19	775.71	763.36	750.82
10.00	38.93	815.33	802.29	789.02
11.00	37.42	854.60	839.71	825.08
12.00	33.97	889.31	873.67	857.98
13.00	33.20	925.48	906.87	889.55
14.00	35.13	960.60	942.00	925.73
15.00	33.97	991.30	975.97	963.00
16.00	34.17	1022.17	1010.14	999.00
17.00	32.21	1052.63	1042.35	1031.78
18.00	28.65	1081.03	1070.99	1060.58

- Output frequency over tuning voltage range
- Caution: Temperature sensitivity

# Overview


---

- Functional Block Concept
- Oscillator Review
- Basic Performance Metrics
- **Methods of Tuning**
- Advanced Performance Metrics
- Conclusion

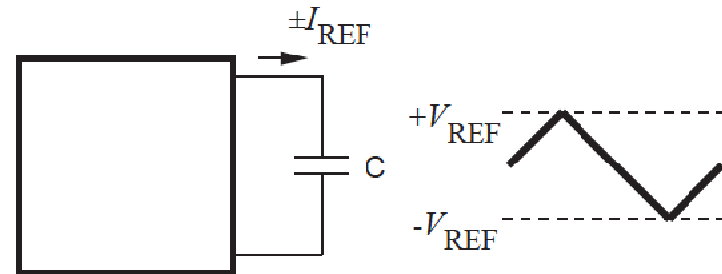
# VCOs / Methods of Tuning

- Require electrical control of some parameter determining frequency:


- **Multivibrator**
  - Charge / discharge current




- **Ring Oscillator**
  - Gate delay

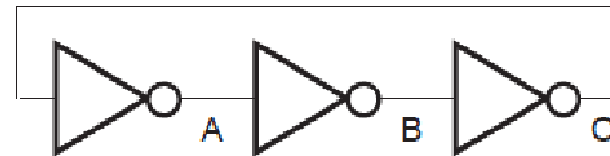

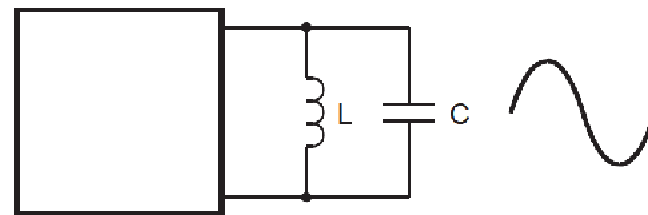- **Resonant**
  - Voltage control of capacitance in LC (varactor)



# Example: Tuning Multivibrator

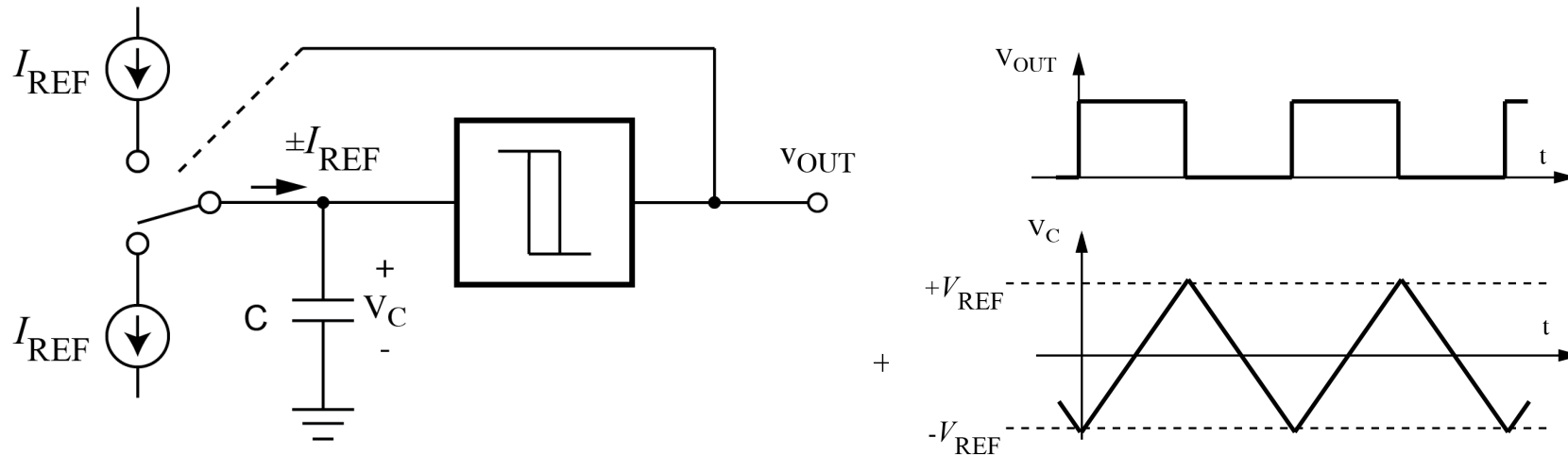

- **Frequency: Controlled by  $I_{REF}$ ,  $C$ ,  $V_{REF}$  thresholds**
- **Use linear transconductance  $G_M$  to develop  $I_{REF}$  from  $V_{TUNE}$**

$$f_{OSC} = \frac{I_{REF}}{4CV_{REF}}$$



$$I_{REF} = G_M V_{TUNE}$$

+ **Very linear  $V_{TUNE} - f_{OSC}$  characteristic**

$$f_{OSC} = \left( \frac{G_M}{4CV_{REF}} \right) V_{TUNE}$$

- **But: poor phase noise;  $f_{OSC}$  limited to MHz range**

# Tuning LC Resonator: Varactor

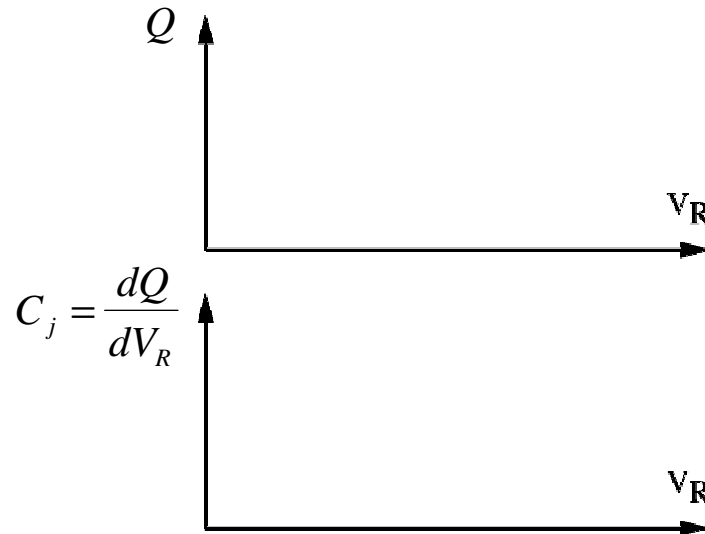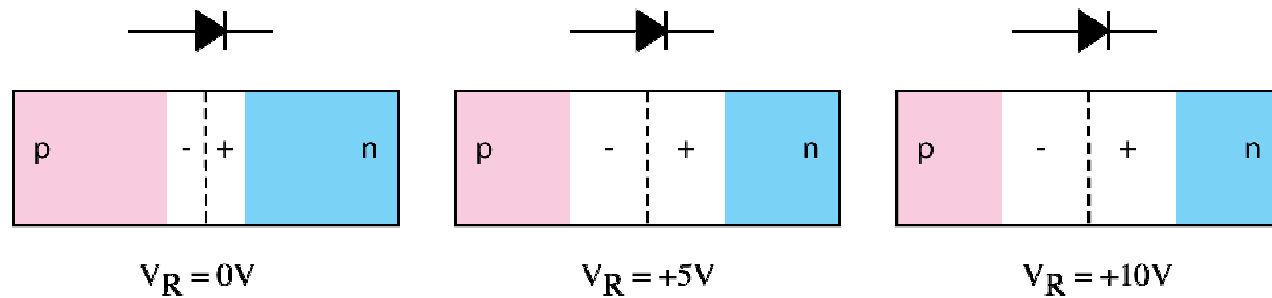


$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_R}{V_{bi}}\right)^m}$$

- Q-V characteristic of pn junction
- Use reverse bias diode for C in resonator
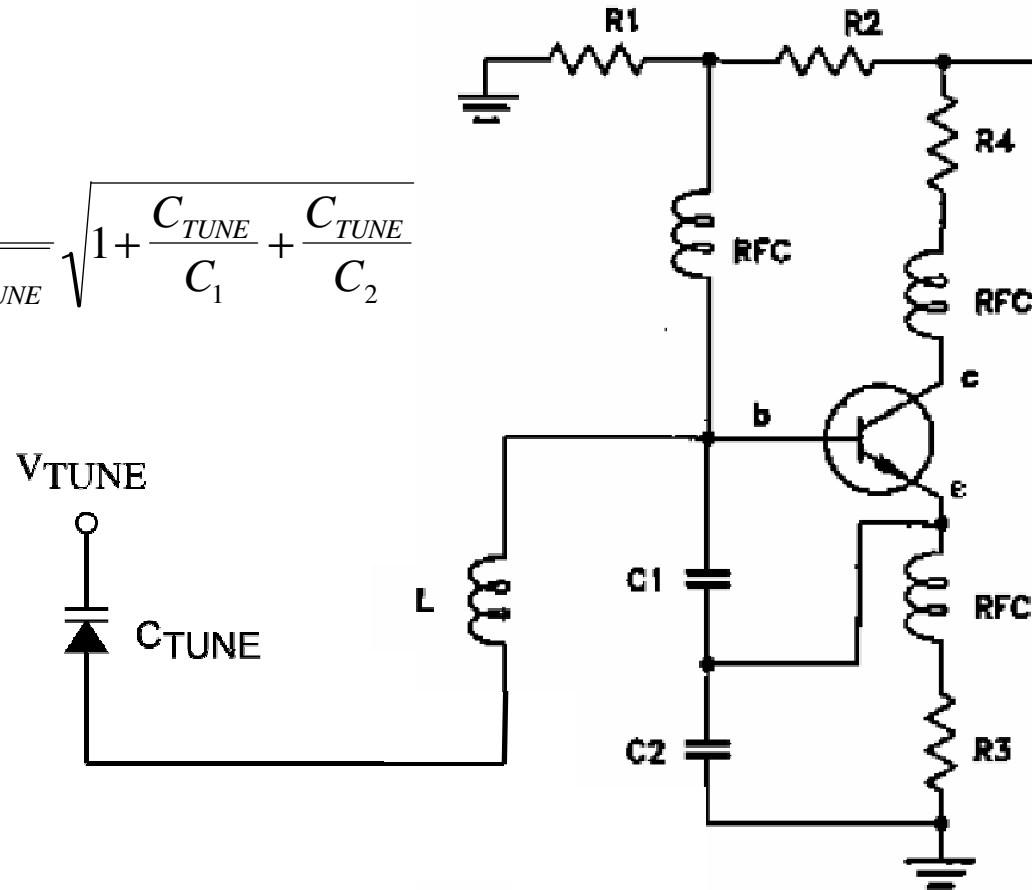
# Example: Clapp oscillator

$$f_{osc} = \frac{1}{2\pi\sqrt{LC_{TUNE}}} \sqrt{1 + \frac{C_{TUNE}}{C_1} + \frac{C_{TUNE}}{C_2}}$$



- Tuning range  $f_{MIN}$ ,  $f_{MAX}$  set by  $C_{TUNE}$  maximum, minimum
- Want  $C_1, C_2 > C_{TUNE}$  for wider tuning range

# Overview

---

- Functional Block Concept
- Oscillator Review
- Basic Performance Metrics
- Methods of Tuning
- **Advanced Performance Metrics**
  - **Tuning Sensitivity**
  - **Phase Noise**
  - **Supply Pushing**
  - **Load Pulling**
- Conclusion



# Advanced Performance Metrics

## VOLTAGE CONTROLLED OSCILLATORS 50 Ω

12.5 MHz to 3 GHz



MODEL PREFIX	FREQUENCY (MHz)		POWER OUTPUT (dBm)	TUNE VOLTAGE (V)		PHASE NOISE (dBc/Hz) SSB@ offset frequencies: Typ.				PULLING (MHz) pk-pk @12 dB	PUSHING (MHz/V)	TUNING SENSITIVITY (MHz/V)	HARMONICS (dBc)		3dB MOD. BANDWIDTH (kHz)	POWER SUPPLY	
	Min.	Max.		Typ.	Min.	Max.	1 kHz	10 kHz	100 kHz				1 MHz	Typ.		Typ.	Typ.

### LINEAR TUNING Wideband

JCOS-175LN	125	175	+3.7	1.0	17.0	-95	-118	-138	-158	0.08	0.05	3-5	-25	-20	2900	12.0	20
JCOS-820BLN	807	832	+3.0	1.0	14.0	-88	-112	-132	-151	0.4	0.4	6.0	-24	-20	2000	10.0	25
JCOS-820WLN	780	860	+9.0	0.0	20.0	-90	-112	-132	-150	4.5	0.3	8.0	-13	-8	2000	9.0	25
JCOS-1100LN	1079	1114	+8.5	0.0	20.0	-88	-110	-130	-150	7.5	0.5	4.5	-15	-10	2000	8.0	25
JTOS-25	12.5	25	+8.0	1.0	11.0	-95	-115	-135	-155	0.03	0.02	1.0-4.0	-26	-13	130	12.0	20
JTOS-50	25	47	+8.5	1.0	15.0	-88	-108	-127	-147	0.06	0.04	2.0-2.6	-19	-12	50	12.0	20
JTOS-75	37.5	75	+8.0	1.0	16.0	-89	-110	-130	-140	0.15	0.11	2.8-4.0	-27	-20	125	12.0	20
JTOS-100	50	100	+8.3	1.0	16.0	-83	-108	-128	-140	0.6	0.2	3.7-4.8	-35	-20	100	12.0	18
JTOS-150	75	150	+9.5	1.0	16.0	-82	-106	-127	-147	0.8	0.3	5.8-6.7	-23	-17	112	12.0	20
JTOS-200	100	200	+10.0	1.0	16.0	-84	-105	-124	-145	1.0	0.2	6-10	-25	-20	110	12.0	20
JTOS-300	150	280	+9.0	1.0	16.0	-82	-102	-122	-142	1.0	0.2	9-14	-28	-20	120	12.0	20
JTOS-400	200	380	+9.0	1.0	16.0	-82	-102	-122	-142	1.4	0.4	10.5-17.1	-25	-20	130	12.0	20
JTOS-535	300	525	+9.5	1.0	16.0	-75	-97	-117	-137	2.0	0.5	10-24	-28	-20	115	12.0	20
JTOS-765	485	765	+8.0	1.0	16.0	-75	-98	-118	-138	2.0	0.5	20-30	-30	-20	100	12.0	20
JTOS-850WW	400	850	+6.0	0.5	18.0	-74	-96	-116	-136	6.0	1.5	15-80	-20	—	185	5.0	20
JTOS-1000W	500	1000	+7.0	1.0	18.0	-73	-94	-114	-134	5.0	1.0	30-40	-26	-20	100	12.0	25

# Tuning Sensitivity

Surface Mount

## Voltage Controlled Oscillator

JTOS-1000W+

Wide Band 500 to 1000 MHz

### Features

- wide frequency range, 500 to 1000 MHz typ.
- 3 dB modulation bandwidth 100 kHz typ.
- octave, linear tuning
- low phase noise, -134 dBc/Hz at 1 MHz offset, typ.
- excellent harmonic suppression, -26 dBc typ.
- aqueous washable

### Applications

- test instruments-signal generators
- wideband frequency synthesizers
- agile communications systems
- catv distribution and set-top convertors
- cellular up and down converters
- digital cordless phones



CASE STYLE: BK377  
PRICE: \$21.95 ea. QTY (5-49)


**+RoHS Compliant**

The +Suffix identifies RoHS Compliance. See our web site for RoHS Compliance methodologies and qualifications

### Electrical Specifications

FREQUENCY (MHz)		POWER OUTPUT (dBm)	TUNING VOLTAGE (V)		PHASE NOISE (dBc/Hz) SSB at offset frequencies: Typ.				PULLING pk-pk @ 12 dB (MHz)	PUSHING (MHz/V)	TUNING SENSITIVITY (MHz/V)	HARMONICS (dBc)		3 dB MODULATION BANDWIDTH (MHz)	DC OPERATING POWER	
Min.	Max.	Typ.	Min.	Max.	1 kHz	10 kHz	100 kHz	1 MHz	Typ.	Typ.	Typ.	Typ.	Max.	Typ.	Vcc (volts)	Current (mA) Max.
500	1000	+7.0	1.0	18	-73	-94	-114	-134	5.0	1.0	30-40	-26	-20	0.1	12	25

# Frequency Range

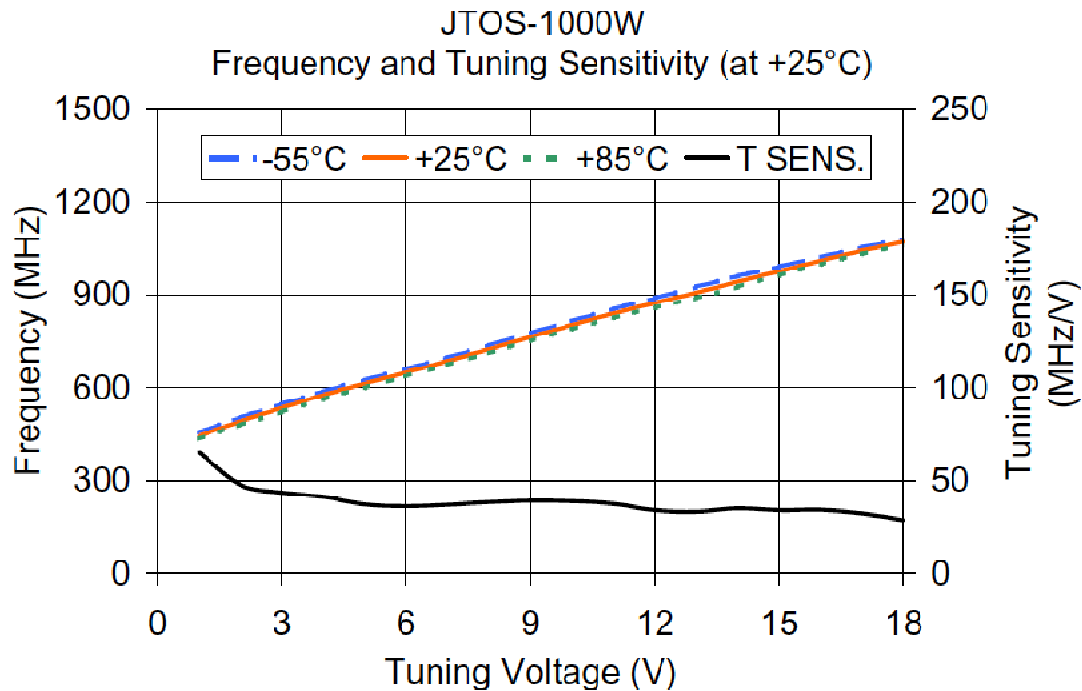

V TUNE	TUNING SENS. (MHz/V)	FREQUENCY (MHz)		
		-55°C	+25°C	+85°C
1.00	65.31	455.40	443.44	433.76
2.00	47.64	503.88	491.08	480.00
3.00	43.38	546.43	534.46	521.76
4.00	41.23	587.53	575.68	562.24
5.00	37.18	624.47	612.87	600.23
6.00	36.00	660.47	648.87	636.80
7.00	36.98	697.54	685.84	673.93
8.00	38.32	736.41	724.17	711.94
9.00	39.19	775.71	763.36	750.82
10.00	38.93	815.33	802.29	789.02
11.00	37.42	854.60	839.71	825.08
12.00	33.97	889.31	873.67	857.98
13.00	33.20	925.48	906.87	889.55
14.00	35.13	960.60	942.00	925.73
15.00	33.97	991.30	975.97	963.00
16.00	34.17	1022.17	1010.14	999.00
17.00	32.21	1052.63	1042.35	1031.78
18.00	28.65	1081.03	1070.99	1060.58

- Change in slope [MHz/V] over tuning voltage range

# Tuning Sensitivity


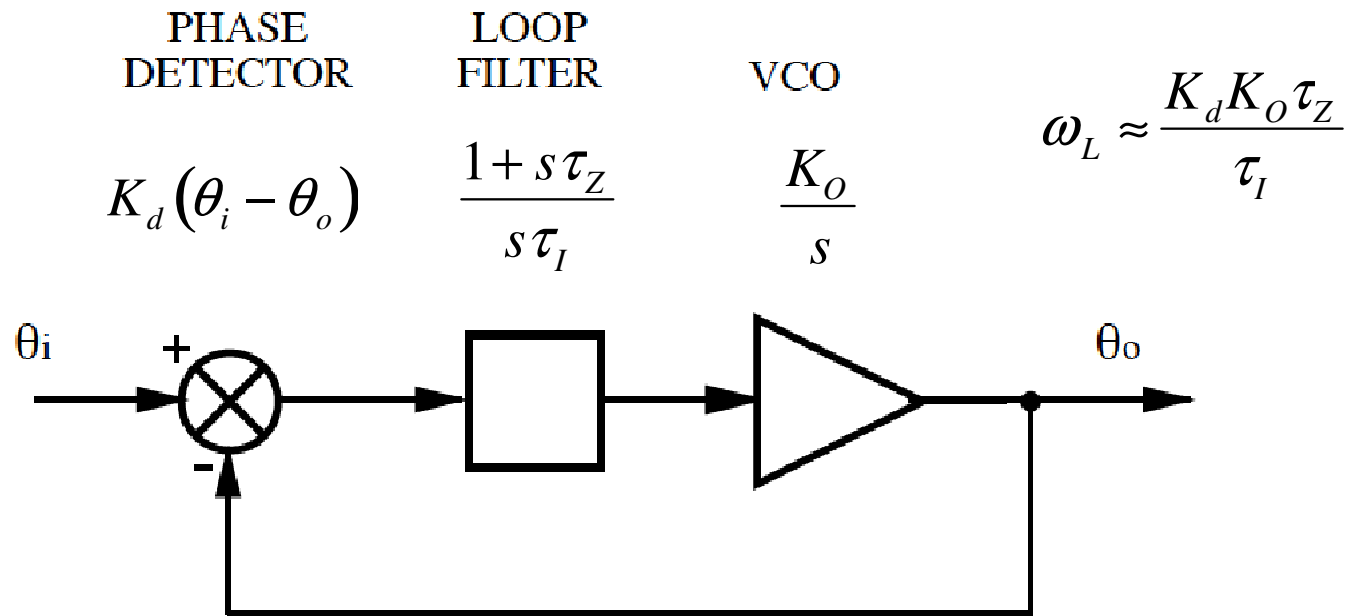


Fig. 3.5. Phaselock loop as a control system.


- Why do you care?
  - PLL: Tuning sensitivity  $K_O$  affects control parameters
  - Loop bandwidth  $\omega_L$  (may not be critical)
  - Stability (critical!)
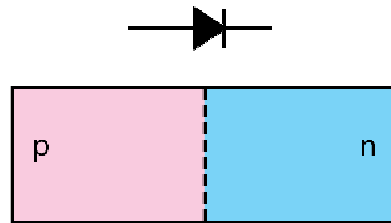
# Varactor Tuning

$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_{TUNE}}{V_{bi}}\right)^m}$$



$$f_{osc} = \frac{1}{2\pi\sqrt{LC}}$$

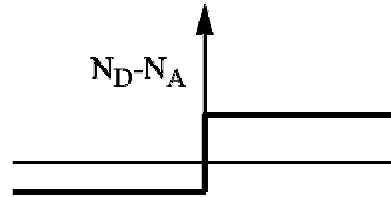

$$f_{osc} \approx \frac{1}{2\pi\sqrt{LC_{j0}}} \left(\frac{V_{TUNE}}{V_{bi}}\right)^{m/2} \quad m = 1/2$$



- **Disadvantages of abrupt junction C-V characteristic ( $m=1/2$ )**
  - **Smaller tuning range**
  - **Inherently nonlinear  $V_{TUNE} - f_{OSC}$  characteristic**

# Hyperabrupt Junction Varactor



$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_{TUNE}}{V_{bi}}\right)^m}$$

$$f_{osc} = \frac{1}{2\pi\sqrt{LC}}$$
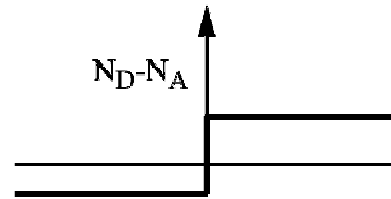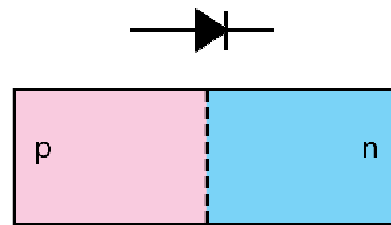
$$f_{osc} \approx \frac{1}{2\pi\sqrt{LC_{j0}}} \left(\frac{V_{TUNE}}{V_{bi}}\right)^{m/2}$$



$$m = 1/2$$

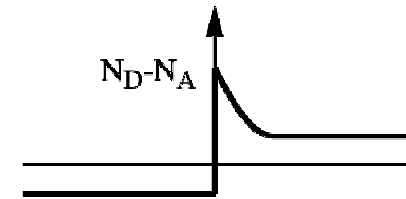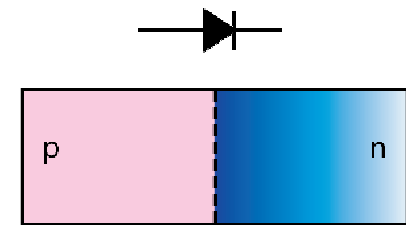

$$m \rightarrow 2$$

- **Hyperabrupt junction C-V characteristic ( $m \approx 2$ )**
  - + **Larger tuning range; more linear  $V_{TUNE} - f_{OSC}$**
  - **Disadvantage: Lower Q in resonator**

# Phase Noise

Surface Mount

## Voltage Controlled Oscillator

JTOS-1000W+

Wide Band 500 to 1000 MHz

### Features

- wide frequency range, 500 to 1000 MHz typ.
- 3 dB modulation bandwidth 100 kHz typ.
- octave, linear tuning
- low phase noise, -134 dBc/Hz at 1 MHz offset, typ.
- excellent harmonic suppression, -26 dBc typ.
- aqueous washable

### Applications

- test instruments-signal generators
- wideband frequency synthesizers
- agile communications systems
- catv distribution and set-top convertors
- cellular up and down converters
- digital cordless phones



CASE STYLE: BK377  
PRICE: \$21.95 ea. QTY (5-49)


**+RoHS Compliant**

The +Suffix identifies RoHS Compliance. See our web site for RoHS Compliance methodologies and qualifications

### Electrical Specifications

FREQUENCY (MHz)		POWER OUTPUT (dBm)	TUNING VOLTAGE (V)		PHASE NOISE (dBc/Hz) SSB at offset frequencies: Typ.				PULLING pk-pk @ 12 dB (MHz)	PUSHING (MHz/V)	TUNING SENSITIVITY (MHz/V)	HARMONICS (dBc)		3 dB MODULATION BANDWIDTH (MHz)	DC OPERATING POWER	
Min.	Max.	Typ.	Min.	Max.	1 kHz	10 kHz	100 kHz	1 MHz	Typ.	Typ.	Typ.	Typ.	Max.	Typ.	Vcc (volts)	Current (mA) Max.
500	1000	+7.0	1.0	18	-73	-94	-114	-134	5.0	1.0	30-40	-26	-20	0.1	12	25


# Phase Noise

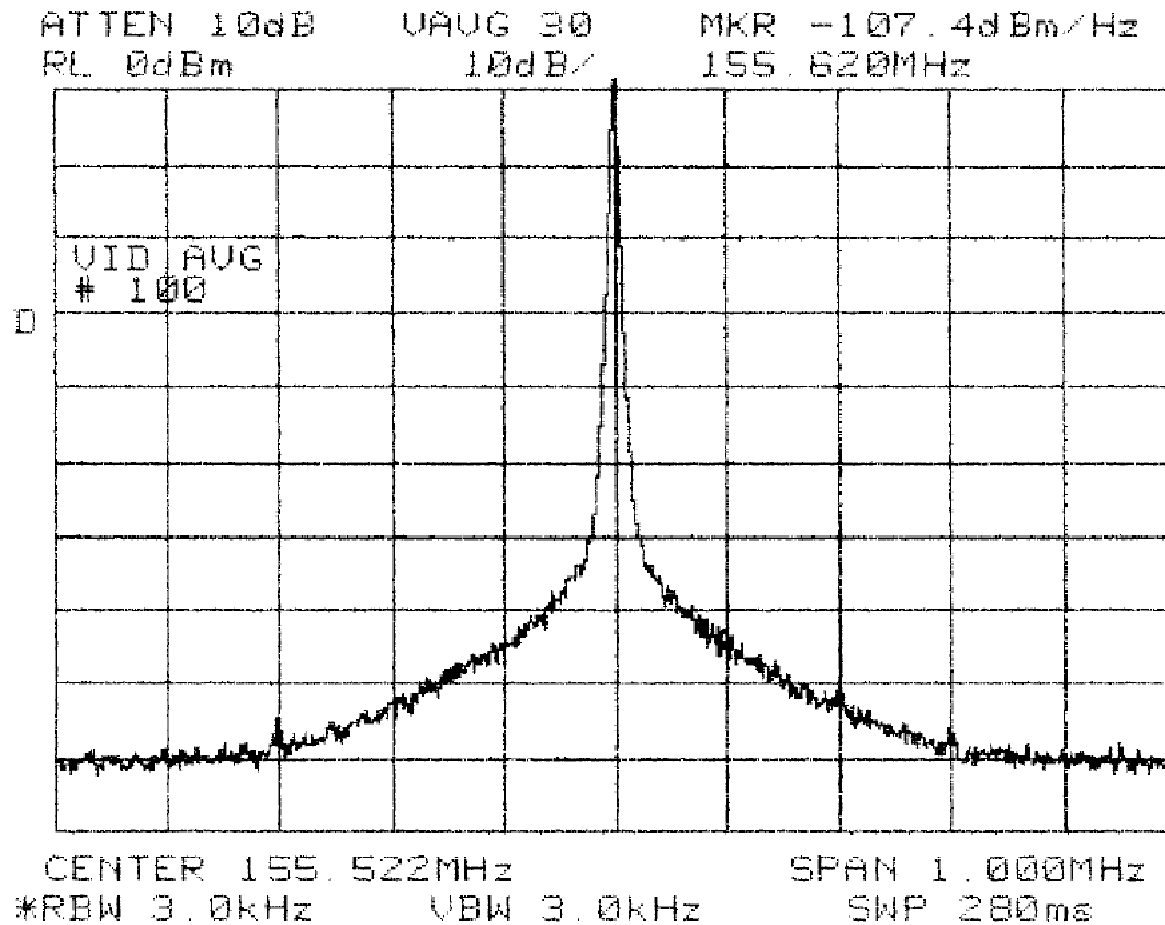

- Power spectrum “close in” to carrier




# Phase Noise: RF System

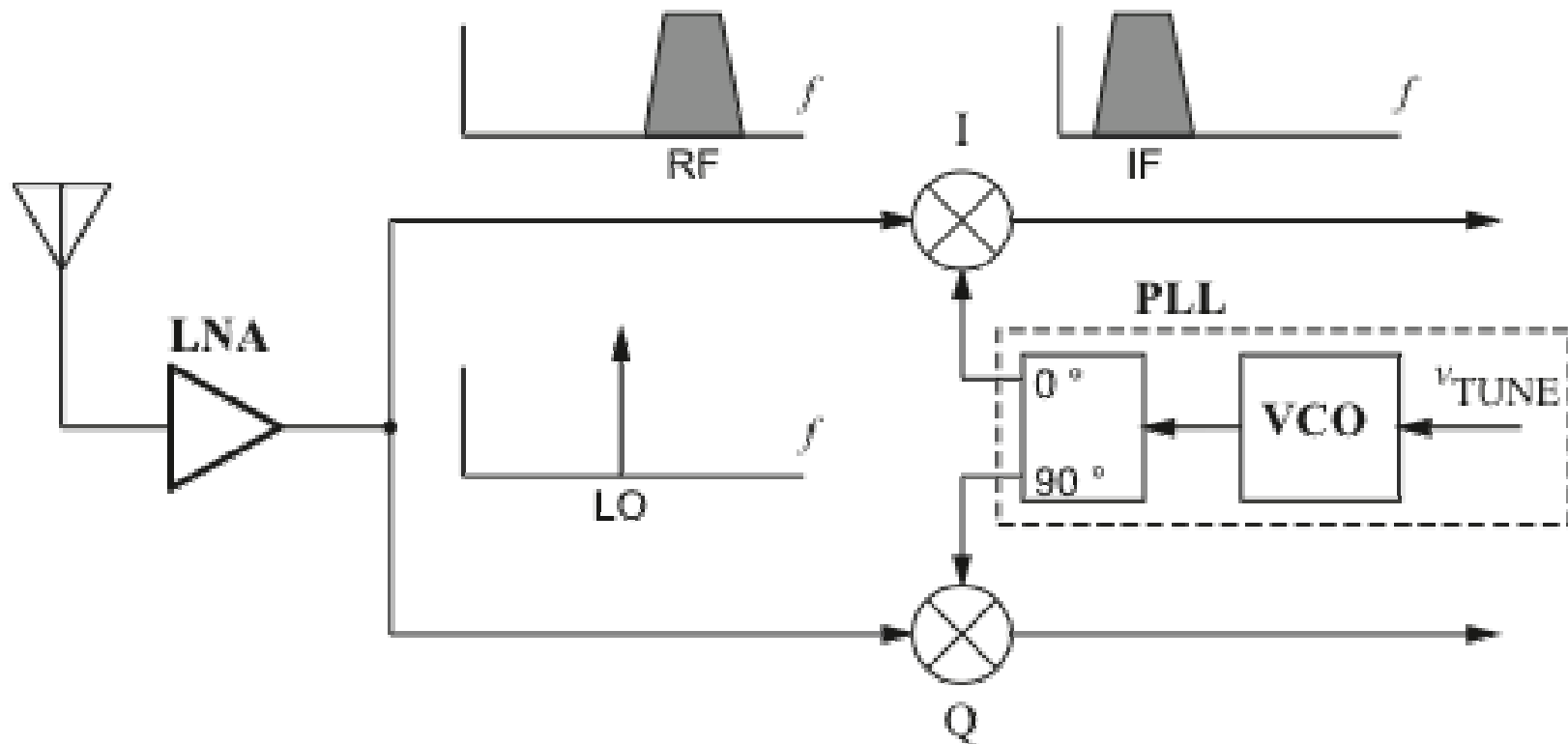


- Mixers convolve LO spectrum with RF
- Phase noise “blurs” IF spectrum

# Phase Noise: Digital System

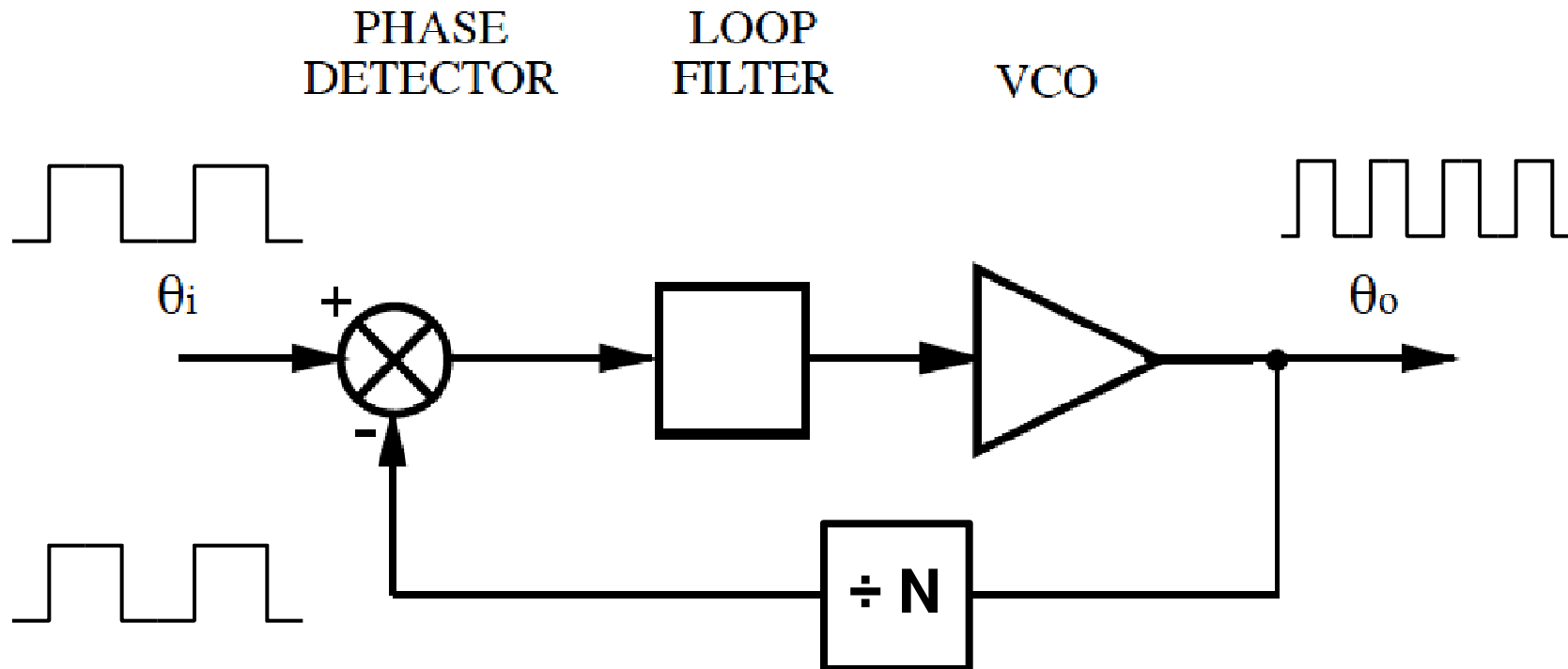


- Time domain jitter on synthesized output clock
- Decreases timing margin for system using clock

# Shape of Phase Noise Spectrum

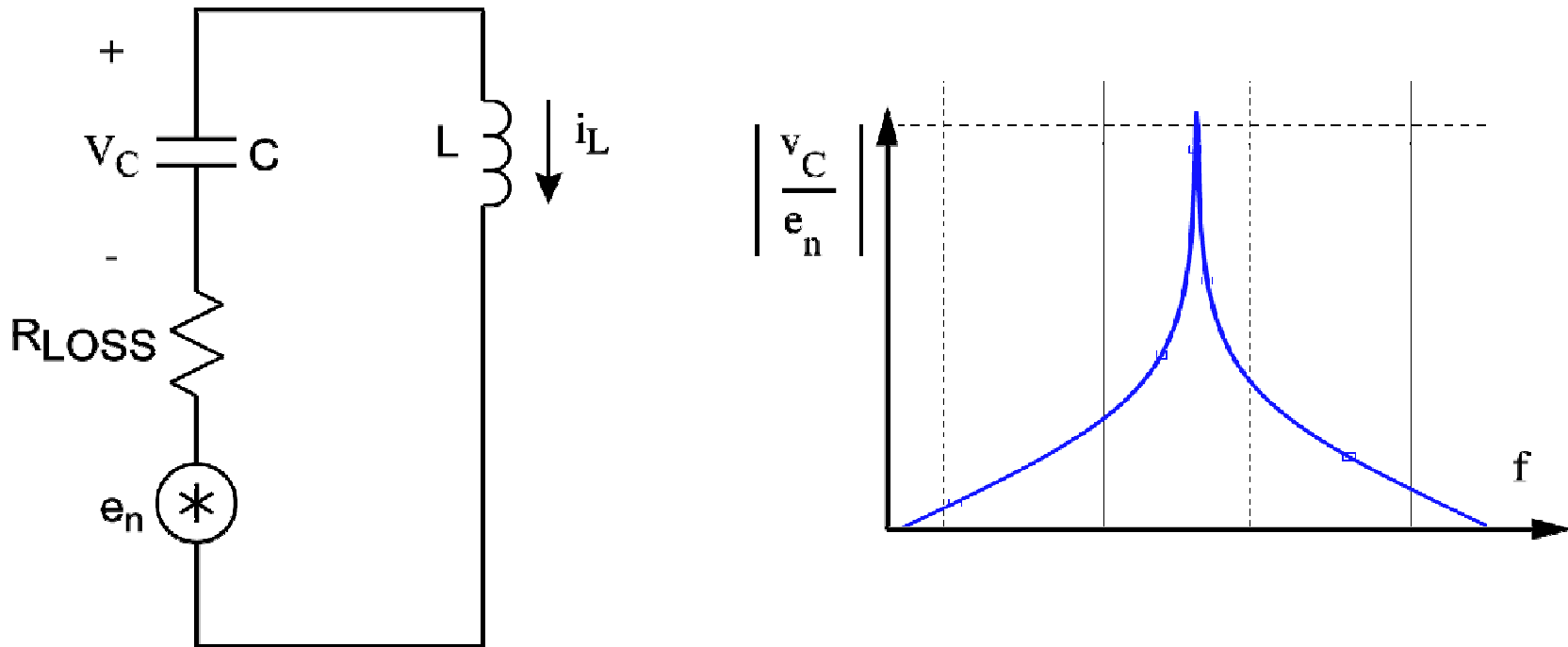


- **LC filters noise into narrow band near fundamental**
- **High Q resonator preferred to minimize noise**

# Phase Noise: Intuitive view

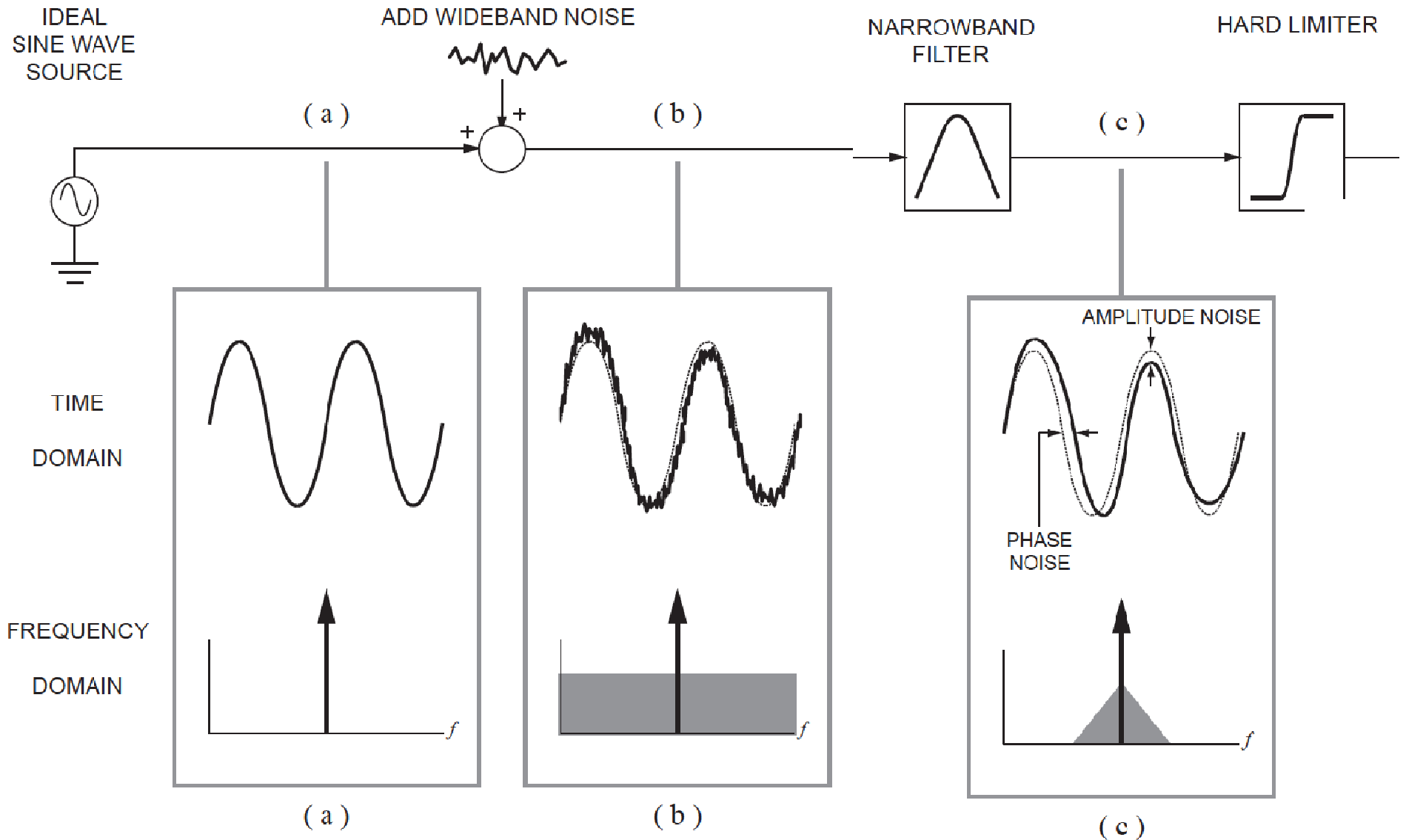


# Phase Noise: Intuitive view

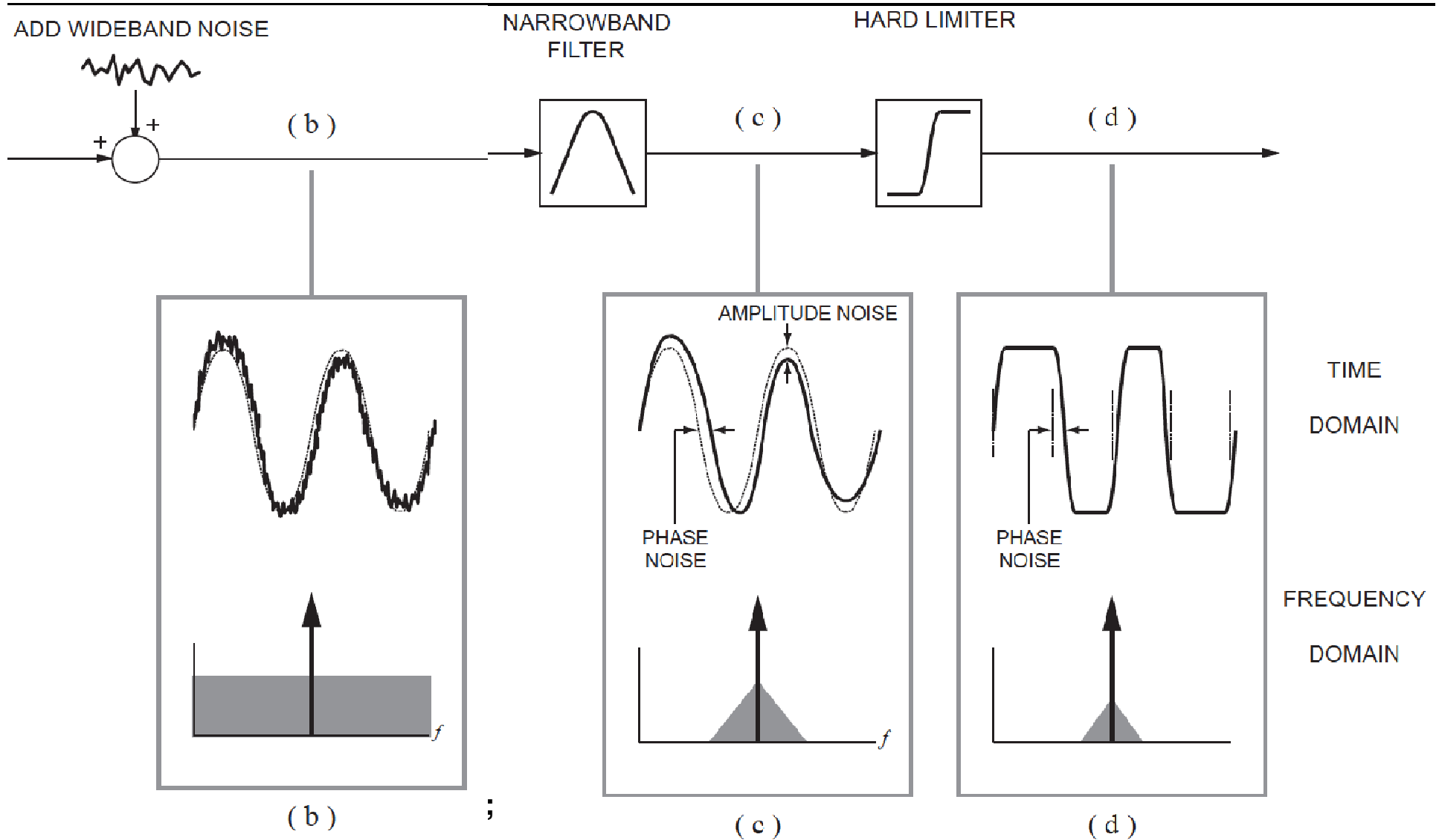
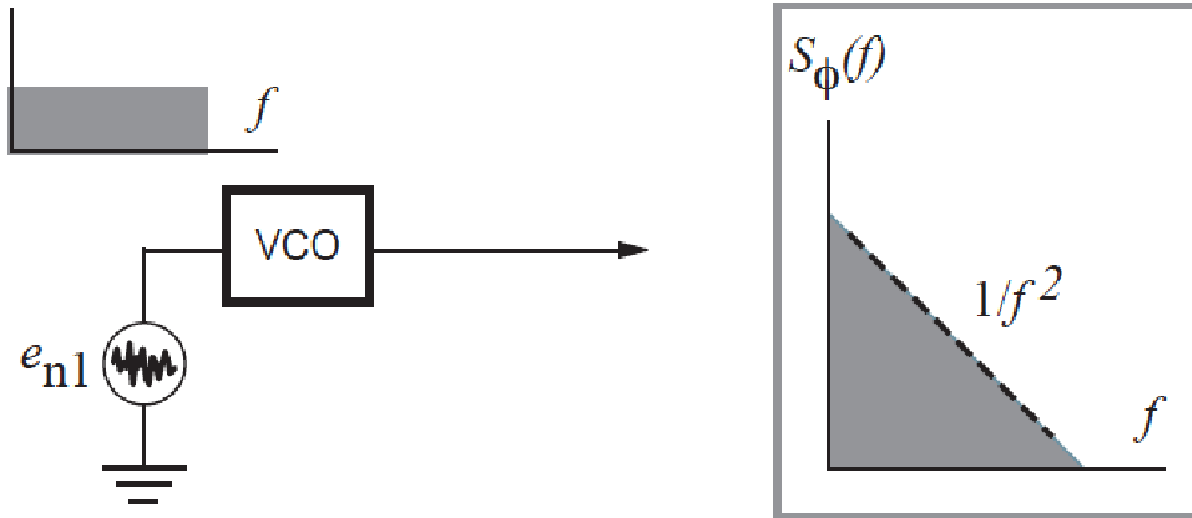
# Phase Noise Description

$S_{n1}(f)$  (a) Ideal white noise at VCO input



- **Symmetric; look at single sided representation**
- **Normalized to carrier: dBc**
- **At different offset frequencies from carrier**
- **White frequency noise: phase noise with -20dB/decade slope**
- **Other noise processes change slope; 1/f noise gives -30dB/decade**


# Phase Noise Specification

Surface Mount


## Voltage Controlled Oscillator

PHASE NOISE  
(dBc/Hz)  
SSB at offset frequencies:  
Typ.

1 kHz	10 kHz	100 kHz	1 MHz
-73	-94	-114	-134

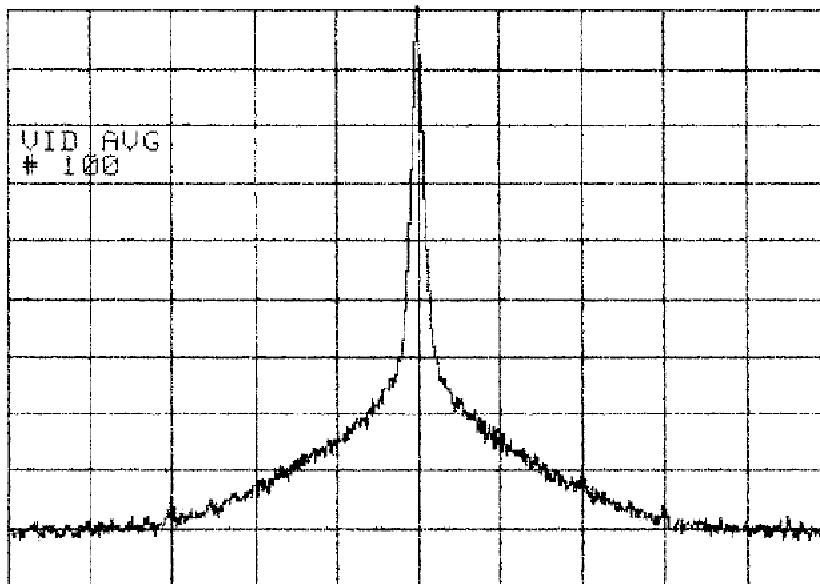


$S_{\phi}(f)$

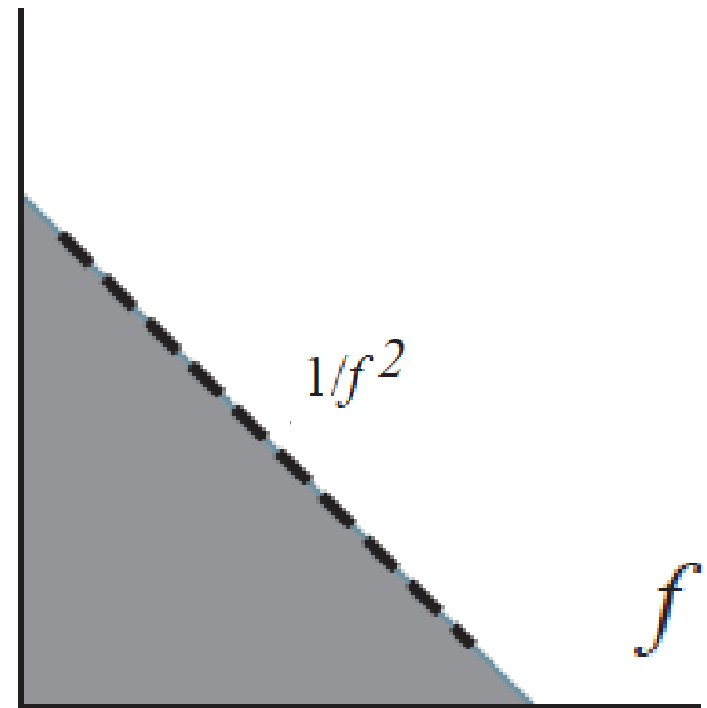

# Sources of Phase Noise

White noise in  $V_{TUNE}$  signal path

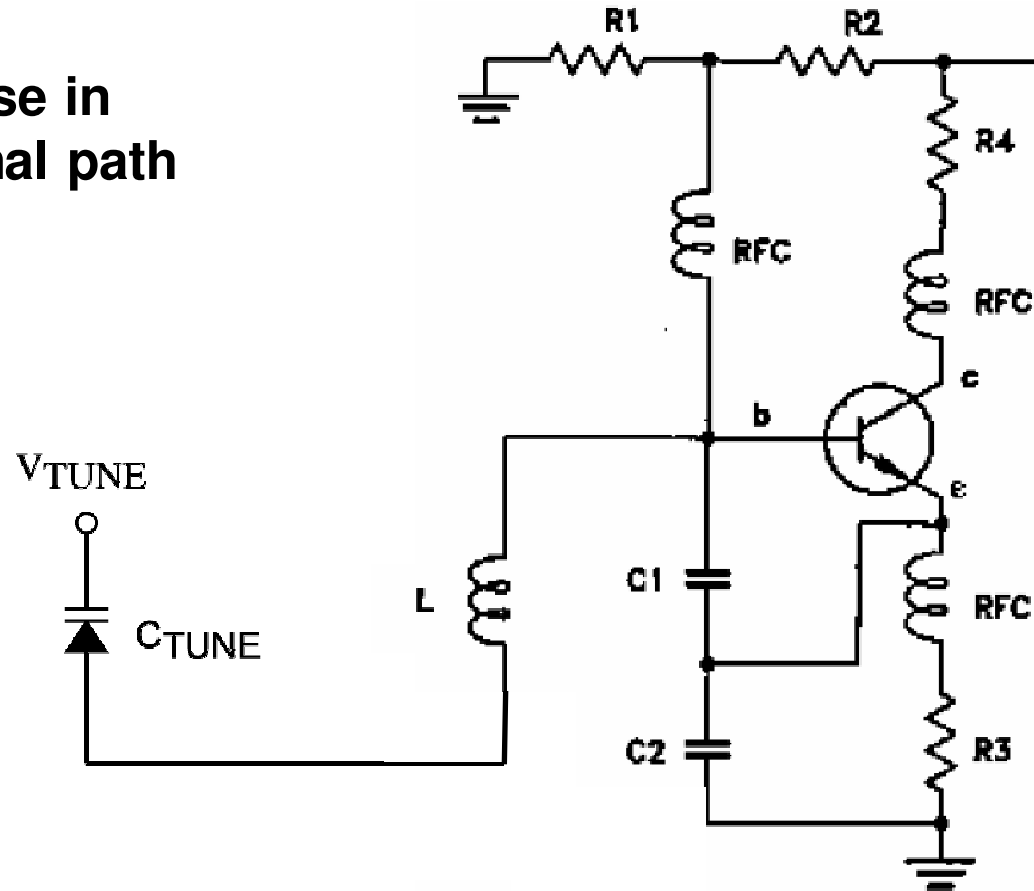


Noise of active devices

Thermal noise: Losses in resonator, series R of varactor




# Supply / Load Sensitivity

---

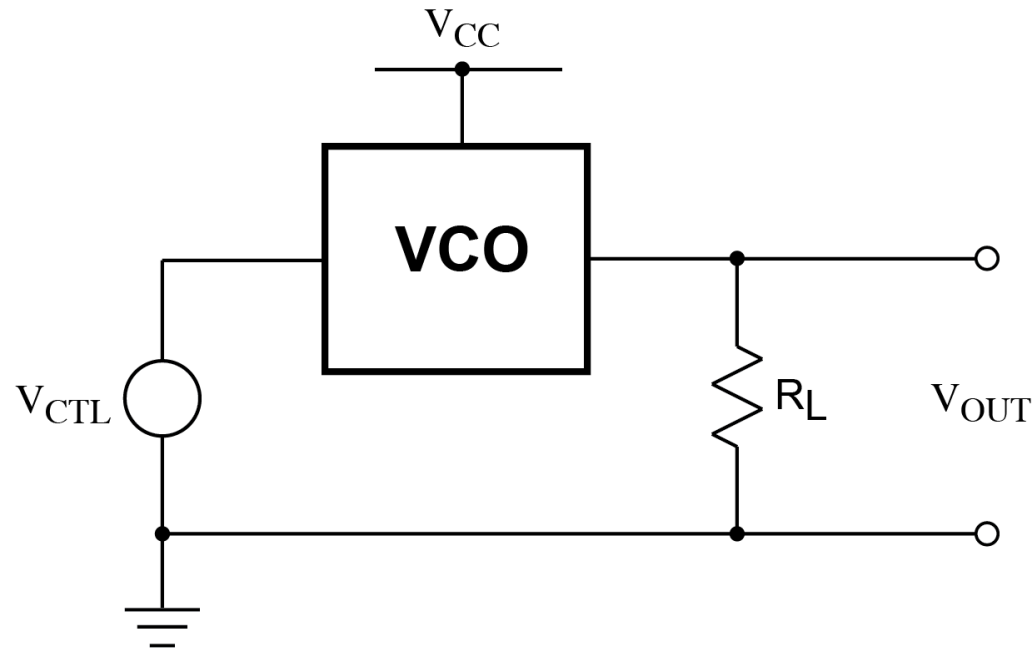


- Ideally tuning voltage is the only way to change output frequency
  - In reality other factors involved
  - Mechanism depends on specifics of circuit
- Power supply dependence: Supply Pushing
- Impedance mismatch at output: Load Pulling

# Supply Pushing

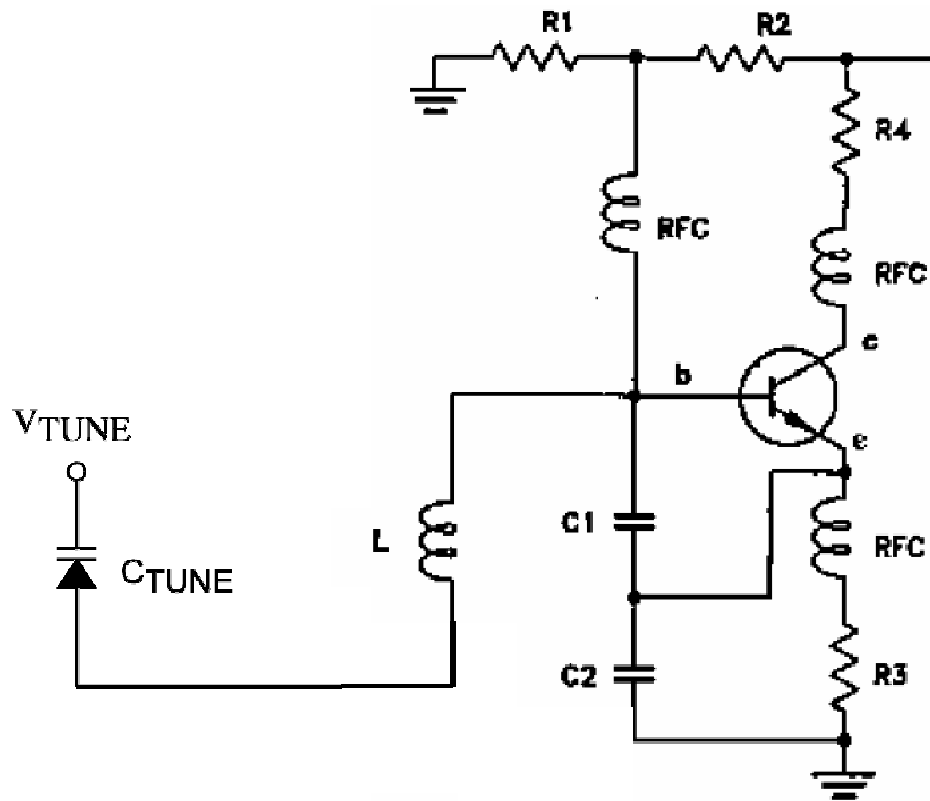

- Change in  $f_{osc}$  due to change in supply voltage
- Clapp oscillator: supply affects transistor bias condition, internal signal amplitudes

# Load Pulling

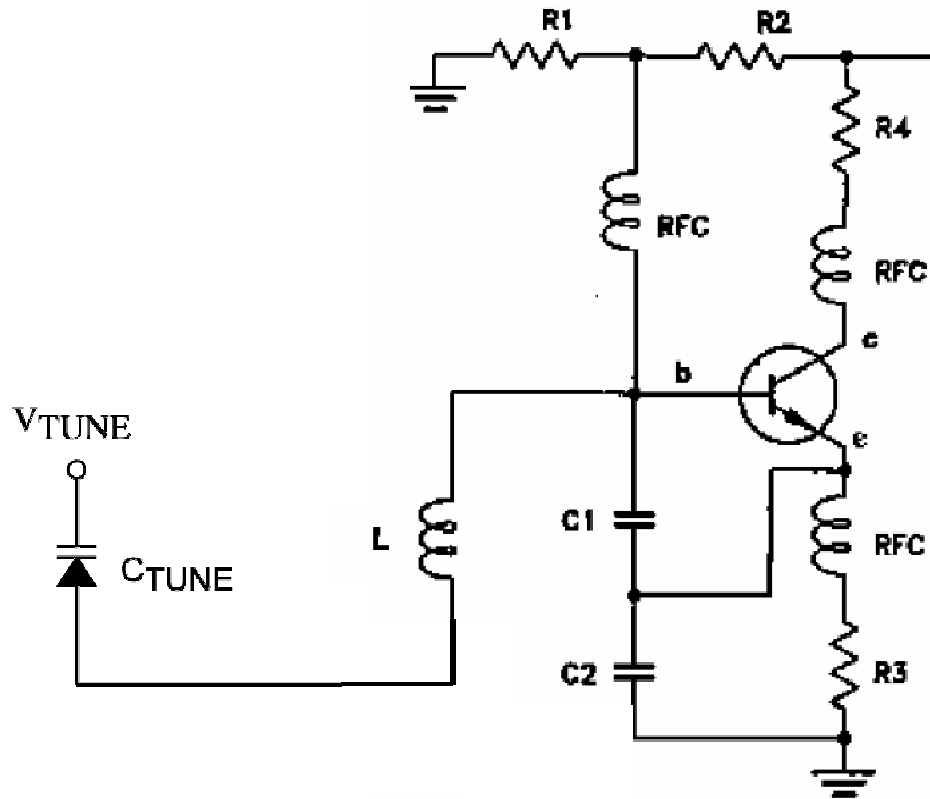

- Change in  $f_{osc}$  due to impedance mismatch at output
- Clapp oscillator; reflection couples through transistor parasitic to LC resonator

# Overview

---

- **Functional Block Concept**
- **Oscillator Review**
- **Basic Performance Metrics**
- **Methods of Tuning**
- **Advanced Performance Metrics**
- **Conclusion**

# Summary: VCO Fundamentals

---

- **First order behavior**
  - Tuning voltage  $V_{\text{TUNE}}$  controls output frequency
  - Specify by min/max range of  $f_{\text{OSC}}$ ,  $V_{\text{TUNE}}$
- **Performance limitations**
  - Linearity of tuning characteristic
  - Spectral purity: phase noise, harmonics
  - Supply, load dependence
- **Different VCO architectures trade frequency range, tuning linearity, phase noise performance**

# Questions?

---

Thank you to our presenter John McNeill and our sponsor Mini-Circuits